

**High-Performance Analog Products**

# **Analog Applications Journal**

**Fourth Quarter, 2007**



© Copyright 2007 Texas Instruments

**[www.BDTIC.com/TI](http://www.BDTIC.com/TI)**

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Management	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>

### Applications

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Broadband	<a href="http://www.ti.com/broadband">www.ti.com/broadband</a>
Digital control	<a href="http://www.ti.com/digitalcontrol">www.ti.com/digitalcontrol</a>
Military	<a href="http://www.ti.com/military">www.ti.com/military</a>
Optical Networking	<a href="http://www.ti.com/opticalnetwork">www.ti.com/opticalnetwork</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Telephony	<a href="http://www.ti.com/telephony">www.ti.com/telephony</a>
Video & Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
Wireless	<a href="http://www.ti.com/wireless">www.ti.com/wireless</a>

Mailing Address: Texas Instruments  
Post Office Box 655303  
Dallas, Texas 75265

# Contents

<b>Introduction</b> .....	4
<b>Data Acquisition</b>	
Using a touch-screen controller's auxiliary inputs .....	5
Most touch-screen controllers (TSCs) have one or more auxiliary analog inputs that can be used to monitor battery voltage or other voltage signals in addition to the TSC signals. This article describes typical applications for these auxiliary inputs. Also discussed are design considerations for ESD protection, circuit isolation after power down, and input-voltage ranges accepted by several devices.	
<b>Power Management</b>	
Driving a WLED does not always require 4 V .....	9
This article investigates the myth that a boost converter is always required to drive white-light-emitting diodes (WLEDs). Several typical WLED datasheets are examined, revealing that many applications require far less than the maximum-rated LED voltage. This article also shows that many applications can be driven by an LDO-based LED driver, such as the Texas Instruments TPS75105, for an extremely small and efficient solution.	
Host-side gas-gauge-system design considerations for single-cell handheld applications .....	12
A host-side gas gauge offers economic advantages in systems with interchangeable battery packs since it eliminates most redundant pack components. This article covers the problems of existing gas gauges and the benefits of Impedance Track™ technology. Also included are design considerations for a host-side gas-gauge and battery-charging system.	
Using a buck converter in an inverting buck-boost topology .....	16
The most common power-supply source for electronic devices has a positive output relative to ground. Some applications like audio amplifiers, line drivers/receivers, and instrumentation amplifiers may require a negative supply relative to ground. This article describes how to use a buck converter to obtain a negative supply output. Included are discussions of basic buck topology, inverting buck-boost topology, and design considerations required to obtain a stable negative power source.	
<b>Index of Articles</b> .....	20
<b>TI Worldwide Technical Support</b> .....	24

**To view past issues of the**  
***Analog Applications Journal*, visit the Web site**  
**[www.ti.com/aaaj](http://www.ti.com/aaaj)**

# Introduction

*Analog Applications Journal* is a collection of analog application articles designed to give readers a basic understanding of TI products and to provide simple but practical examples for typical applications. Written not only for design engineers but also for engineering managers, technicians, system designers and marketing and sales personnel, the book emphasizes general application concepts over lengthy mathematical analyses.

These applications are not intended as “how-to” instructions for specific circuits but as examples of how devices could be used to solve specific design requirements. Readers will find tutorial information as well as practical engineering solutions on components from the following categories:

- Data Acquisition
- Power Management

Where applicable, readers will also find software routines and program structures. Finally, *Analog Applications Journal* includes helpful hints and rules of thumb to guide readers in preparing for their design.

# Using a touch-screen controller's auxiliary inputs

By Wendy Fang, *Precision Analog Applications, High-Performance Analog*,  
and Tony Chang, *Precision Analog Nyquist, High-Performance Analog*

## Introduction

Texas Instruments (TI) touch-screen controllers (TSCs), including the ADS7843/45/46, TSC2046, and TSC2003/4/5/6/7, have touch-screen input pins and one or more non-touch-screen or auxiliary analog input pins, such as the battery-voltage-monitoring pin ( $V_{BAT}$ ) of the TSC2046 or the AUX pin of the TSC2007. These auxiliary inputs make it possible to monitor the system's battery level or other voltage signals by sharing time with touch-screen inputs or using time periods when the touch screen is not touched.

The auxiliary analog inputs of different TI TSCs may have different input ranges and different levels of electrostatic-discharge (ESD) protection, so certain requirements or

limitations should be considered when they are used. This article discusses the general and specific features and limitations of the TSC auxiliary (including battery-voltage) inputs.

## Auxiliary analog inputs

Table 1 lists auxiliary analog input pins of TI's current TSCs. Inside a TSC, a MUX selects and connects one of the analog inputs to the ADC via commands sent through the SPI or I<sup>2</sup>C ports. Figure 1 shows an example.


## Auxiliary input mode

TI's TSCs can be operated in either differential or single-ended (SE) input mode, but auxiliary analog inputs can be measured and converted only in SE mode (see Figure 2).


**Table 1. Auxiliary analog input(s) of TI TSC devices**

TSC	AUXILIARY ANALOG INPUTS		$V_{REF}$	MAIN FEATURES <sup>1</sup>
	NUMBER OF INPUTS	PIN NAMES		
ADS7843	2	IN3, IN4	External	4-wire, SPI, command-based
ADS7845	1	AUXIN	External	5-wire, SPI, command-based
ADS7846	2	$V_{BAT}$ , AUX	Internal	4-wire, SPI, command-based
TSC2046	2	$V_{BAT}$ , AUX	Internal	4-wire, SPI, command-based
TSC2003	4	$V_{BAT1}$ , IN1, $V_{BAT2}$ , IN2	Internal	4-wire, I <sup>2</sup> C, command-based
TSC2004	1	AUX	External	4-wire, I <sup>2</sup> C, register-based
TSC2005	1	AUX	External	4-wire, SPI, register-based
TSC2006	1	AUX	External	4-wire, SPI, register-based
TSC2007	1	AUX	Shared with $V_{DD}$	4-wire, I <sup>2</sup> C, command-based

**Figure 1. Block diagram of TSC's internal input circuit**

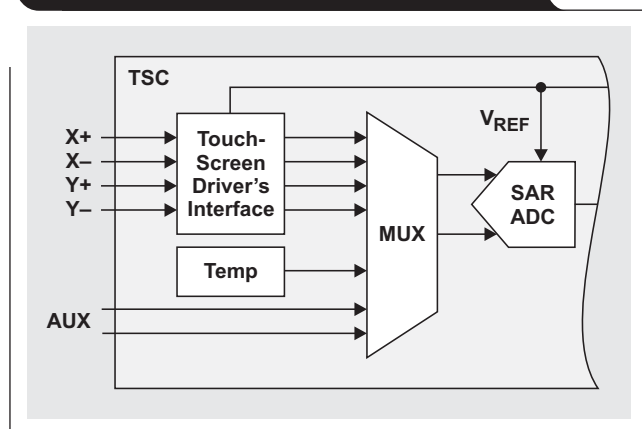

**Figure 2. SE mode of a TSC**

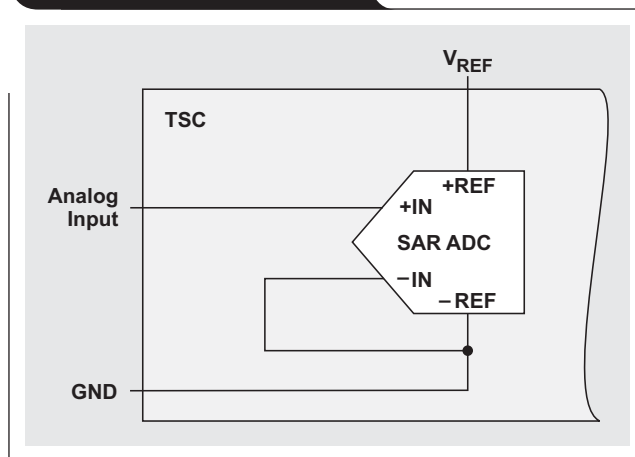

A TSC in differential mode does not need any reference, since the signal's driver is connected to +REF and -REF directly. However, the reference voltage,  $V_{REF}$ , is a must for SE operation and thus is always needed when an auxiliary input, such as the AUX or  $V_{BAT}$ , is measured.

The reference voltage can be provided to the TSC's ADC externally or internally for the ADS7846, TSC2046, and TSC2003. When an external reference is used, these devices can be powered up at the  $V_{CC}$  pin with a supply voltage between 2.2 and 5.25 V, and an external  $V_{REF}$  ranging from 1.0 V to  $V_{CC}$  can be provided. When the TSC's internal reference is used, the ADS7846, TSC2046, or TSC2003 should be powered up with a 2.7- to 5.25-V supply to guarantee that the internal  $V_{REF}$  will be around 2.5 V (2.45 V ~ 2.55 V). Other TI TSCs do not have the built-in voltage reference. In practical applications, one can simply route the same TSC power supply to the reference.

### Auxiliary-input voltage range

The signal range for an auxiliary input should always be within 0 V to  $V_{REF}$ . Signals beyond this range will saturate the ADC and can even increase the temperature, damaging the input circuitry.

The signal range for a battery-monitor input, say  $V_{BAT}$ , can greatly exceed the  $V_{REF}$  level, since there is a voltage divider with each  $V_{BAT}$  pin (see Figure 3). The input divider circuit limits the range of the signal to the ADC to within 0 V to  $V_{REF}$ . Figure 3 shows that the signal to the ADC is only 25% of the signal at the  $V_{BAT}$  pin.

As shown in Table 1, the ADS7846, TSC2046, and TSC2003 have one or two battery-monitor input(s) designed to monitor/measure signals of up to 6.0 V while the device is powered with much lower voltage, down to 2.7 VDC.

### TSC auxiliary-input features

The main features of TSC auxiliary (including battery) inputs can be summarized as follows:

- Auxiliary input signals can be measured only in SE mode.
- A reference voltage,  $V_{REF}$ , must be provided to the ADC when an auxiliary input is measured.
- The signal range of an auxiliary input must be within 0 V to  $V_{REF}$ .
- The battery input,  $V_{BAT}$ , can range from 0 V to as high as  $4 \times V_{REF}$ , up to 6.0 V.

### Special applications

The following discussion focuses on the special applications of the auxiliary analog input pins of TSCs.

#### Unused input pins

If the TSC's analog input pins are not used, it is recommended that they be connected directly to an analog ground.

#### Using AUX input pin to monitor $V_{BAT}$

As Table 1 shows, several TI TSCs are not furnished with a battery-voltage-monitoring pin ( $V_{BAT}$ ). A regular auxiliary input cannot be used directly for monitoring the battery,

Figure 3. Voltage divider reduces input to ADC


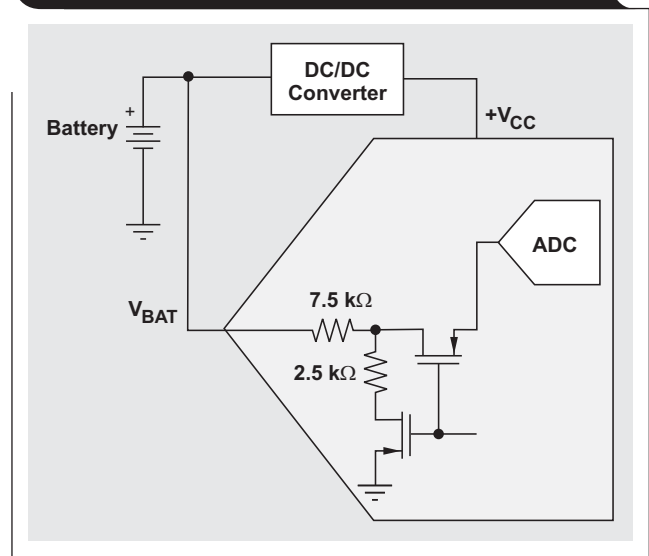


Figure 4. Using AUX with external voltage divider to monitor battery voltage

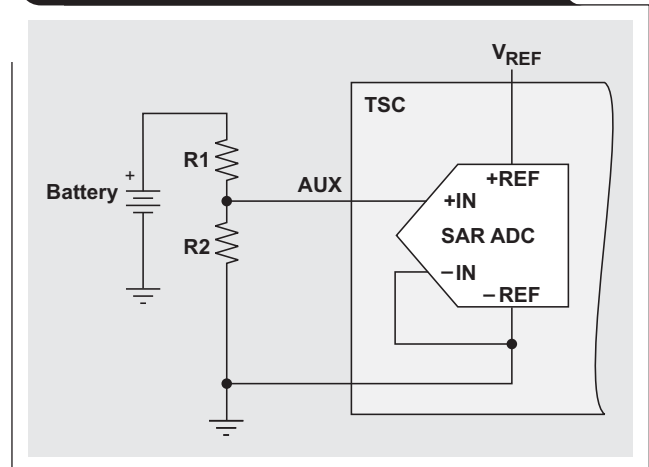


since the battery's voltage is normally higher than that of the TSC's power supply (and thus that of the  $V_{REF}$ ).

A TSC auxiliary pin such as AUX can still be used to measure/monitor the battery voltage if an external voltage divider is added between the battery and the AUX, as shown in Figure 4. R1 and R2 values should be selected with wide enough margins to ensure that the signal at the AUX pin is within 0 V to  $V_{REF}$ . Note that the voltage divider shown in Figure 4 consumes extra power since a current of  $V_{CC}/(R1 + R2)$  continuously drains the battery. Larger resistance can reduce power consumption.

The  $V_{BAT}$  input circuit of TI TSCs does not consume extra power from the battery since there is a switcher between the divider and the power (ground) (see Figure 3), and the internal divider is powered up only during the short period of battery measurement.

**Figure 5. Using TSC AUX pin to monitor battery with controllable switch**

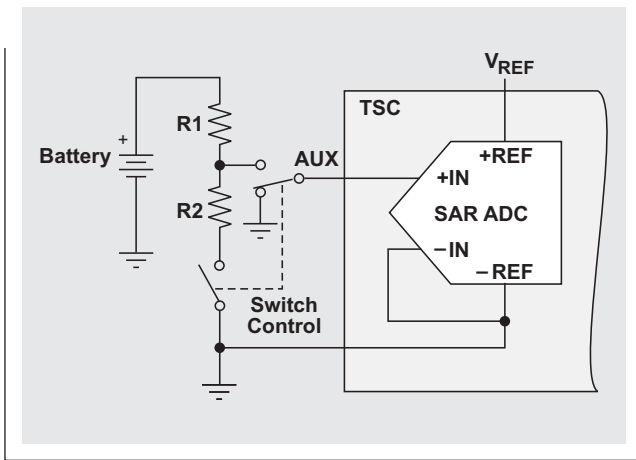


Similarly, while a TSC's AUX pin is used to monitor battery voltage, adding a controllable switcher like that shown in Figure 5 can reduce power consumption and ensure disconnection of the signal from the AUX pin while the TSC is powered down.

**ESD protection and auxiliary-input requirements during power down**

It is very common in practical applications to power down a TSC when it is not in use to reduce system power consumption. A question then arises: Can the analog signal stay connected to the TSC when the TSC's power source is removed?

Figure 6 shows one case in which the analog input should be removed before the TSC is powered down. If


**Figure 6. External ESD-protection circuit may supply pseudo power to TSC**

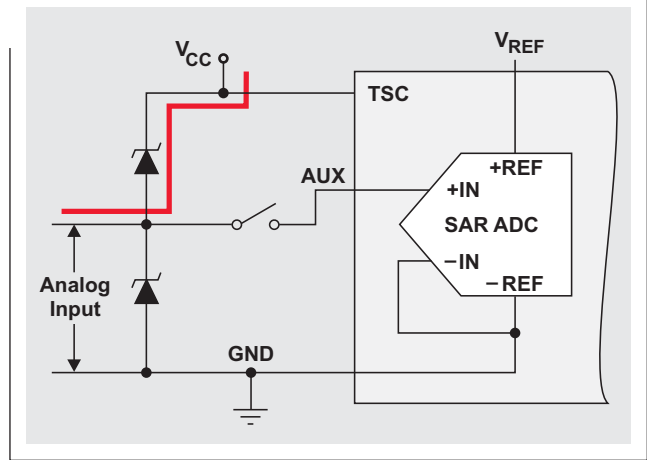


the analog input signal is active (AUX is nonzero) when the TSC is powered down ( $V_{CC} = 0$ ), the analog signal may be routed to the  $V_{CC}$  through the ESD-protection diode (see the red line in Figure 6). This may partially or fully power up the TSC, depending upon the amplitude of the input signal, consuming more power and possibly causing the TSC to malfunction. Thus the circuit configuration in Figure 6 should be avoided.

An alternative is to simply use ESD-protection circuitry as shown in Figure 7. Under extremely large electrostatic voltages, the circuit in Figure 7a may not be as efficient as that in Figure 7b due to the limited current flow through the ESD-protection diodes. On the other hand, the circuit in Figure 7b is not symmetric and therefore does not provide equal protection for positive and negative ESD bursts.


**Figure 7. ESD-protection circuits for TSC analog input pin**

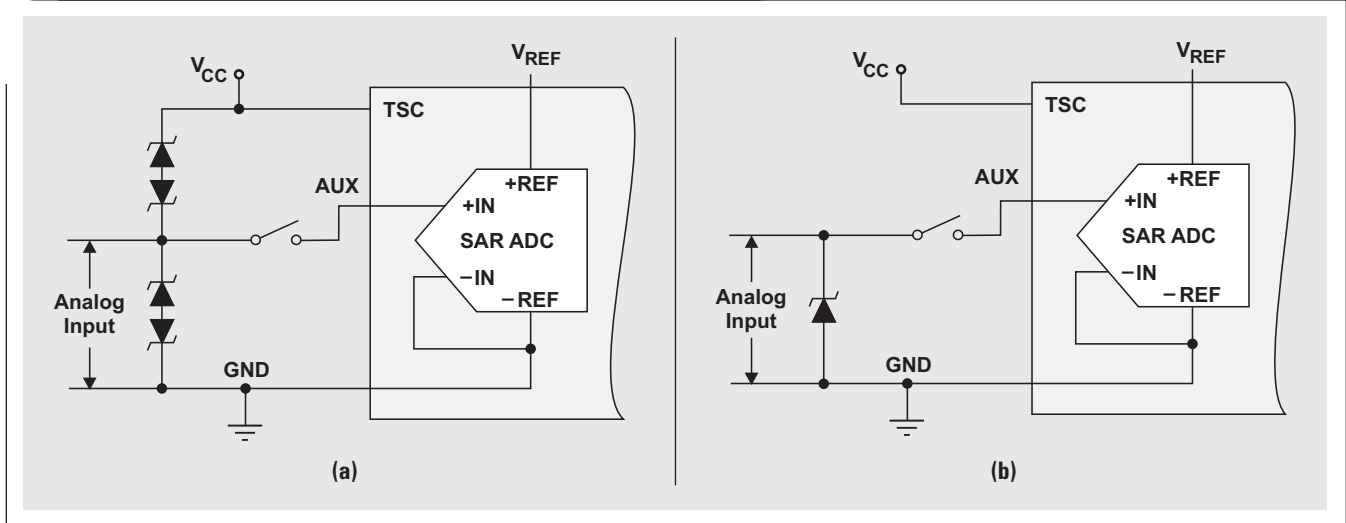

**Figure 8. TSC2004/5/6/7 internal ESD protection for AUX input**

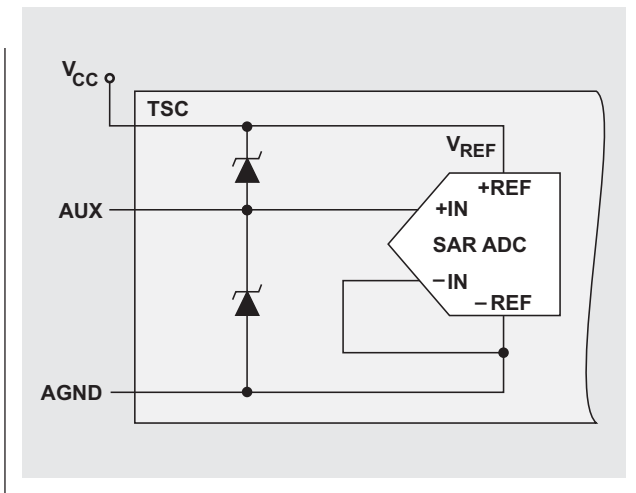

**Figure 9. Switching off TSC2004/5/6/7 AUX before TSC is powered down**

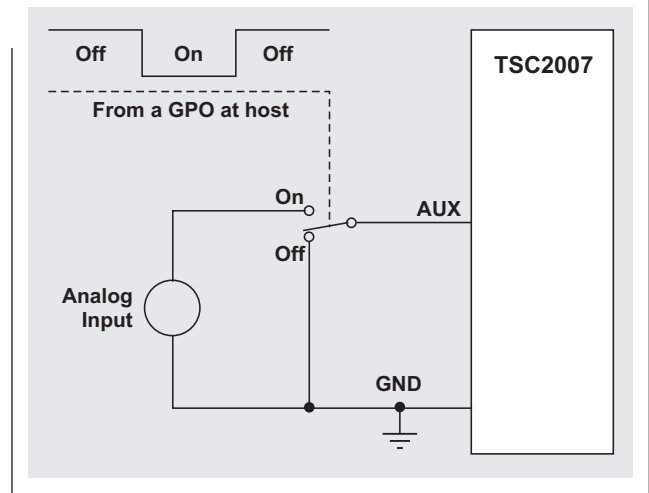

Some of TI's new TSCs, including the TSC2004/5/6/7, were designed with the enhanced, on-chip ESD protection shown by the simplified circuit in Figure 8. Obviously, for these devices, the input signal to the TSC's AUX should be removed before the TSC's  $V_{CC}$  power is shut down. An example of removing the AUX signal is shown in Figure 9.

**Special applications summary**

- An unused analog input pin should be connected directly to the analog ground.
- Pay attention to the divider's resistance values and power consumption when using an AUX to monitor the battery voltage.
- Before removing the TSC's power, always use software commands to disable the TSC's auxiliary functions.
- For the ADS7846, TSC2046, and TSC2003, the nonzero signal to the AUX or  $V_{BAT}$  pin can stay connected while the TSC's power source is removed.
- For the TSC2004/5/6/7, the nonzero signal to AUX should be removed from the analog input pin before the TSC power is removed.

**Reference**

For more information related to this article, you can download an Acrobat Reader file at [www-s.ti.com/sc/techlit/litnumber](http://www-s.ti.com/sc/techlit/litnumber) and replace "litnumber" with the **TI Lit. #** for the materials listed below.

<b>Document Title</b>	<b>TI Lit. #</b>
1. Wendy Fang, "Operation Schemes of Touch Screen Controllers," Application Report . . . . .	.slaa359

**Related Web sites**

[dataconverter.ti.com](http://dataconverter.ti.com)  
[www.ti.com/sc/device/partnumber](http://www.ti.com/sc/device/partnumber)  
 Replace *partnumber* with ADS7843, ADS7845, ADS7846, TSC2003, TSC2004, TSC2005, TSC2006, TSC2007, or TSC2046



# Driving a WLED does not always require 4 V

By Will Hadden

Power Management Products, Portable Power DC/DC Applications

The popularity of white-light-emitting diodes (WLEDs) has skyrocketed, primarily because they are used to provide backlight to portable electronics displays. The common belief is that a single WLED requires a 4-V drive voltage. Since a Li-ion battery provides an average voltage of 3.6 V, the general industry consensus is that a step-up converter is required to power WLEDs from a single-cell Li-ion battery. As a result, many ICs are available for driving WLEDs, most requiring an external inductor or flying capacitors to boost the cell voltage high enough. As WLED technology continues to mature, the forward-voltage requirements continue to drop. Currently, there are many LEDs available with typical forward voltages ( $V_F$ ) in the 3.2- to 3.5-V range with maximum ratings at 3.7 to 4 V. The datasheets usually specify these voltages at LED currents of around 15 to 25 mA. This article discusses lower-current applications and how they affect the forward voltage of the WLED. It also introduces the Texas Instruments (TI) TPS75105, a new LED driver designed to efficiently drive these lower-voltage LEDs with a reduced solution size and cost.


## LED forward voltage

The WLED is similar to other standard p-n junction diodes. It does not conduct current until a sufficient forward voltage has been applied. After the threshold is exceeded, the forward current increases with the forward voltage of the WLED. Typical I-V curves for two WLEDs are shown in Figure 1.

Utilizing these graphs is a simple task. As with typical diode I-V curves, the current rises sharply with the voltage after crossing the threshold. The typical forward voltage for the device in Figure 1a is specified to be 3.2 V at 20-mA forward current with a maximum of 3.7 V over process and temperature variations. This leads to the conclusion that the application requires a step-up DC/DC converter to properly drive the WLED from a single Li-ion cell with an output of 3 to 4.2 V. However, this is not necessarily the case. Take, for example, a 5-mA WLED-current application. The curve in Figure 1a shows that the forward voltage required to drive 5 mA is around 2.9 V, which is much less than the typical voltage required to drive 20 mA as specified in the datasheet. A boost converter is not required to drive a 2.9-V output voltage from a 3.6-V Li-ion cell.

WLEDs are specified with a typical value as well as a maximum value to cover lot-to-lot process and manufacturing variations. The I-V curves provided in the datasheet are usually specified with a part that falls at the typical specification. Although the curve shape is valid for every part that is manufactured, the curve shifts to the right or

Figure 1. Typical WLED I-V curves

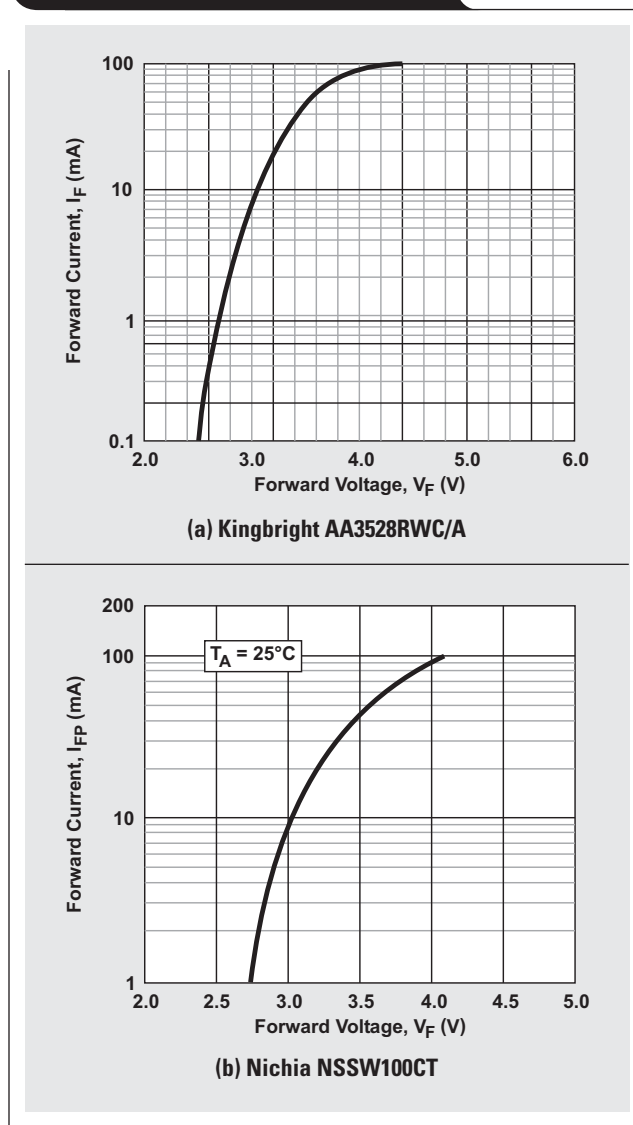

left depending on the forward voltage at the test conditions for that device. If we use another LED with the same part number as in the previous example, the forward voltage measures 3.7 V (the maximum rating) at the typical test conditions (20-mA forward current). This voltage, which is 0.5 V higher than a typical device, translates to a maximum forward voltage of 3.4 V (2.9 V + 0.5 V) required to drive this WLED at 5 mA. Depending on the cutoff voltage of the application, a boost converter is not needed to drive

this particular WLED at 5 mA. This technique makes it easy to determine the maximum forward voltage for any application.

### What about temperature variations?

Some applications require WLEDs to work in harsher conditions with extreme temperatures. Temperature variation affects LED characteristics, but the effect is not as drastic at low current levels as at higher ones. The graph in Figure 2 from a typical WLED datasheet shows forward voltage versus temperature.


This graph shows that the temperature dependence is much stronger with a higher current and forward voltage. Additionally, the forward voltage drops as the temperature increases. The 5-mA curve shows that the forward voltage drops approximately 0.1 V from room temperature (25°C) to the maximum-rated temperature (85°C). This should be taken into account when determining the required forward voltage, but the effect is negligible. If a particular application requires that the LED be driven in a very cold environment, the increased forward voltage may result in lower brightness at low input voltages.

### An ultrasmall LED-driver solution


A typical solution for driving multiple WLEDs is to connect them in series and then drive the series string with either an inductive boost converter or a charge pump. This is an excellent method with higher WLED currents that require a higher forward voltage. However, as previously discussed, a boost converter is not required in every WLED driver application. A simpler and lower-cost driver for low-current WLED applications is the ultrasmall TPS75105 LED driver IC. The TPS75105, a linear current source with an ultralow 28-mV dropout voltage, is used for driving four parallel WLEDs in two separate banks. This device provides four 2%-matched current paths in two separately enabled banks. The device is available in the ultrasmall 9-ball, 1.5-mm<sup>2</sup> wafer-chip-scale package (WCSP), requires no external components when using the default current output, and therefore results in an incredibly small 1.5-mm<sup>2</sup> solution size. In addition, the TPS75105 is one of the most inexpensive WLED lighting solutions that TI offers. The application circuit for the TPS75105 is shown in Figure 3.

At first glance, using a low-dropout linear circuit to drive LEDs may seem impractical, given the linear regulator's reputation for low efficiency. However, the efficiency of LDOs is often misunderstood. LDO efficiency is entirely based on the input/output voltage ratio; therefore, the efficiency of driving WLEDs can be quite high. For example, driving a 3-V WLED from a 3.6-V Li-ion battery input


**Figure 2. Forward voltage vs. temperature (Nichia NSSW100CT)**

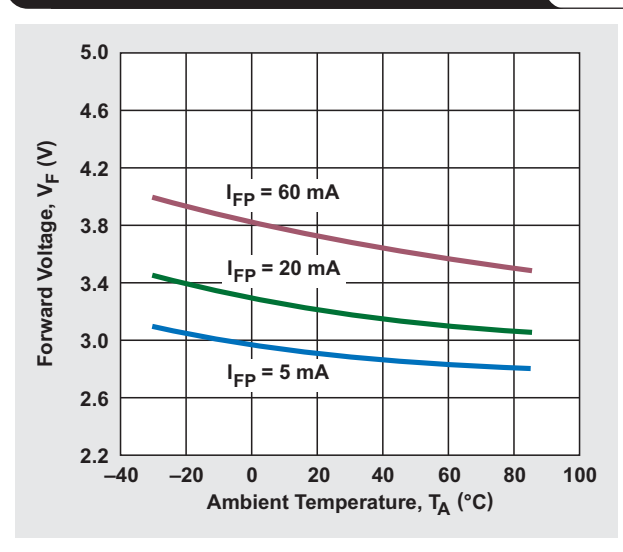

**Figure 3. TPS75105 application circuit**

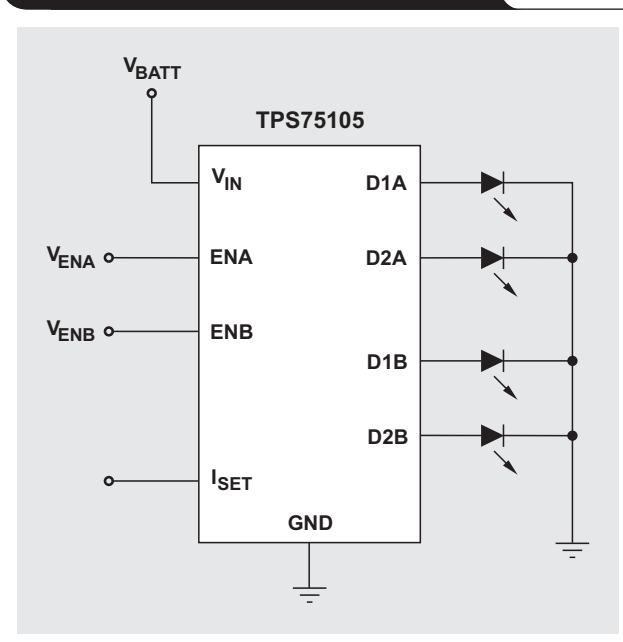

**Figure 4. TPS75105 LED efficiency**

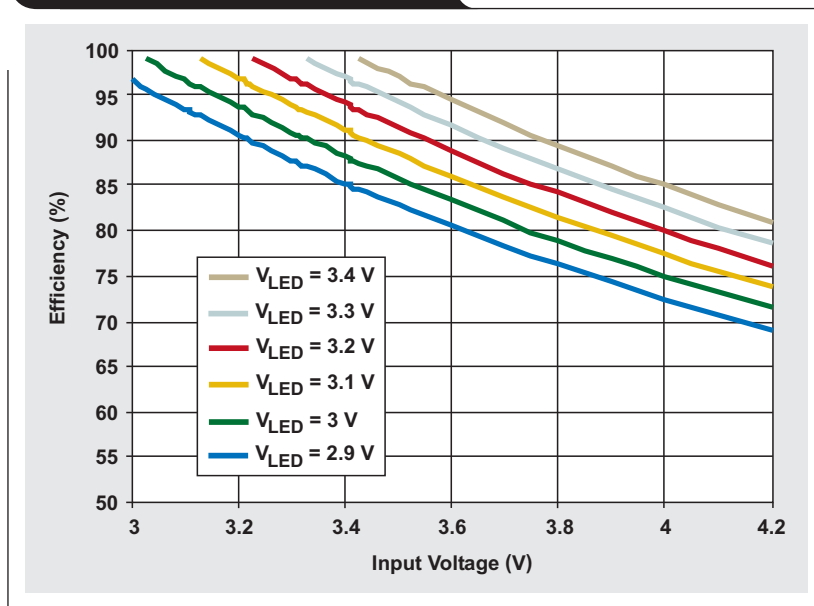


translates into an LED efficiency of 83%. Figure 4 shows the TPS75105 efficiency data for several different WLED forward voltages over the Li-ion battery range. The LED efficiency for the TPS75105 is comparable to or better than that of other WLED-driver solutions.

Figure 5 demonstrates the LED efficiency of the TPS7510x over the Li-ion discharge curve. The average efficiency for the entire discharge range is over 80% for all three curves, and up to 90% when V<sub>LED</sub> = 3.3 V.

While this article concentrates on low-current applications, the TPS7510x can drive up to 25 mA per LED if the input voltage allows. These applications benefit from the very small size.

**Figure 5. TPS7510x LED efficiency over the Li-ion discharge curve**

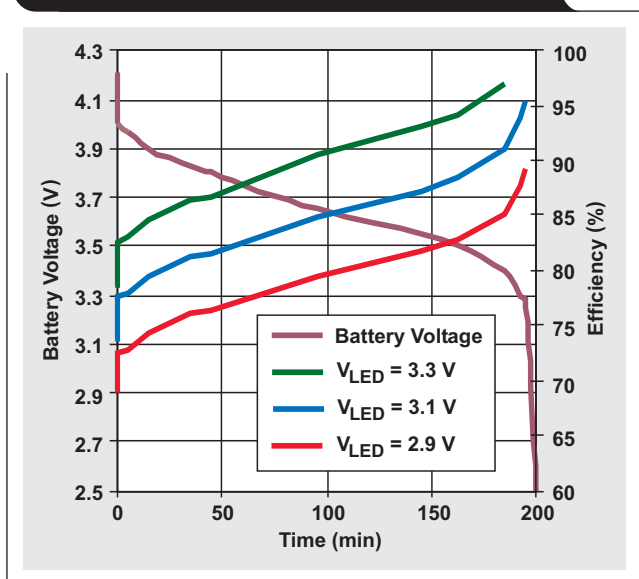

**Conclusion**

When an LED-driver application is evaluated, special consideration should be given to how much current the application requires. If it is well below the current at which the application's WLED V<sub>F</sub> is specified, the WLED datasheet I-V curves should be reviewed to determine the actual V<sub>F</sub> in the application. The application may be able to use a low-dropout linear current source such as the TPS75105 to achieve an ultralow solution size and low cost without sacrificing the efficiency of a switching step-up converter.

**References**

For more information related to this article, you can download an Acrobat Reader file at [www-s.ti.com/sc/techlit/litnumber](http://www-s.ti.com/sc/techlit/litnumber) and replace "litnumber" with the **TI Lit. #** for the materials listed below.

Document Title	TI Lit. #
1. Kingbright Corporation, City of Industry, CA, AA3528RWC/A Datasheet, Spec. No. DSAG3655.	—
2. "Specifications for Nichia Chip Type White LED," Nichia Corporation, NSSW100CT Datasheet, No. STSE-CC6014B.	—
3. "Low Dropout, Two-Bank LED Driver with PWM Brightness Control," TPS7510x Datasheet	.sbvs080
4. TPS75105EVM User's Guide	.slvu182

**Related Web sites**

[power.ti.com](http://power.ti.com)  
[www.ti.com/sc/device/TPS75105](http://www.ti.com/sc/device/TPS75105)

# Host-side gas-gauge-system design considerations for single-cell handheld applications

(This article will be available December 2007)







# Using a buck converter in an inverting buck-boost topology

By John Tucker

Applications Engineer

## Introduction

Most practical electronic devices require an input voltage source. This may be a battery for handheld or portable devices, a 115-V AC line source or “wall wart” for home consumer electronics, or a regulated DC voltage bus for industrial or telecommunications applications. Typically, the input voltage source must be converted to one or more lower voltage sources to power individual circuits such as processors, memory, FPGAs, or other logic. Buck converters are commonly used to derive the required input voltage from a higher voltage source. In some cases, generating a negative voltage from a positive input voltage source may be required. These applications can include audio amplifiers, line drivers and receivers, or instrumentation amplifiers. In such instances it is possible to configure the buck converter into an inverting buck-boost topology, where the output voltage is negative with respect to ground.

## Basic buck topology

To understand the inverting buck-boost circuit operation, first consider the basic topology of the buck converter as shown in Figure 1. The components inside the box with a

blue dotted outline are typically integrated into the converter’s integrated circuit, while those outside are required external components.

When the FET switch is on, the voltage across the inductor is  $V_{IN} - V_{OUT}$ , and the current through the inductor increases at a rate of


$$\frac{di}{dt} = \frac{V_{IN} - V_{OUT}}{L}$$

When the switch is off, the inductor voltage reverses to keep the inductor current continuous. Assuming that the voltage drop across the diode is small, the inductor current ramps down at a rate of  $di/dt = V_{OUT}/L$ . The steady-state load current is always carried by the inductor during both the on and off times of the FET switch. The average inductor current is equal to the load current, and the peak-to-peak inductor ripple current is

$$I_{L(PP)} = \frac{(V_{IN} - V_{OUT})D}{f_{SW}L},$$

where  $V_{IN}$  is the input voltage,  $V_{OUT}$  is the output voltage,  $D$  is the duty cycle  $V_{OUT}/V_{IN}$ ,  $f_{SW}$  is the switching frequency, and  $L$  is the output inductance.

Figure 1. Buck topology

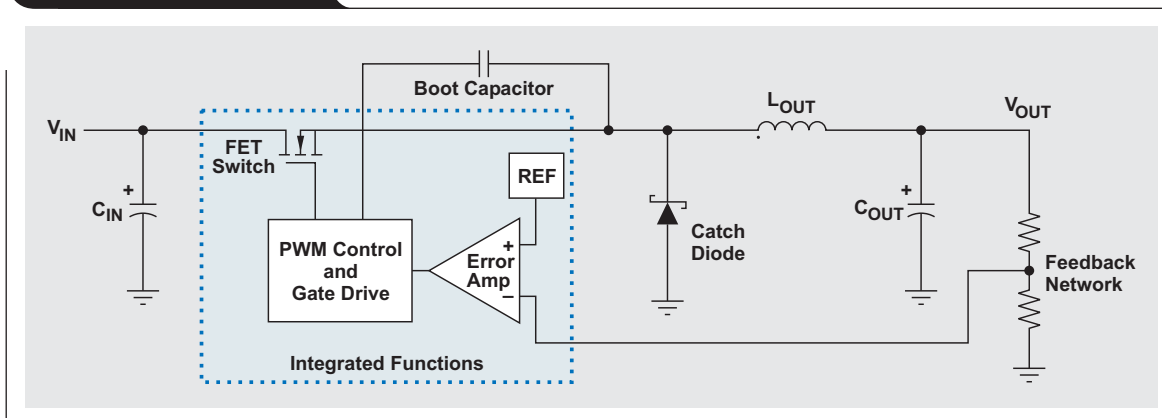



## Inverting buck-boost topology

Compare the preceding operation to that of the inverting buck-boost topology shown in Figure 2. The inductor and catch diode have switched places relative to the buck converter of Figure 1; and the output capacitor is reversed in polarity, as the output voltage is negative. During operation, when the FET switch is on, the voltage across the inductor is  $V_{IN}$  and the current ramps up at a rate of  $di/dt = V_{IN}/L$ . While the FET switch is on, the entire load current is supplied by energy stored in the output capacitor. When the FET switch turns off, the inductor reverses polarity to keep the inductor current continuous. The voltage across the inductor is approximately  $V_{OUT}$ , and the inductor current decreases at a rate of  $di/dt = -V_{OUT}/L$ . During the off time, the inductor supplies current both to the load and to replenish the energy lost by the capacitor during the on time. So for the buck-boost circuit, the average inductor current is

$$I_L = \frac{I_{OUT}}{1-D},$$

and the peak-to-peak inductor current is

$$I_{L(PP)} = \frac{V_{IN}D}{f_{SW}L}.$$

The duty cycle,  $D$ , is approximately

$$D = \frac{V_{OUT}}{V_{IN} + V_{OUT}}.$$

These basic differences in circuit operation are important when the buck converter is used as a buck-boost converter.

## Design considerations

When a nonsynchronous buck converter is used in an inverting buck-boost configuration, certain considerations must be made. The design equations are presented in simplified form with the semiconductors idealized and other component losses neglected. To implement the buck-boost topology of Figure 2, the buck-converter ground pin is connected to  $V_{OUT}$ , and the positive lead of the output capacitor is connected to ground. The voltage across the device's  $V_{IN}$  pin to GND is then  $V_{IN} - (-V_{OUT})$ , rather than

just  $V_{IN}$  as in the buck converter. This combined voltage must be less than the specified  $V_{IN}$  of the chosen device.

The operating duty cycle is

$$D = \frac{V_{OUT}}{V_{OUT} - V_{IN}},$$

and the average inductor current is

$$I_{L(avg)} = \frac{I_{OUT}}{1-D}.$$

These values also differ from those of the buck converter, whose duty cycle,  $D = V_{OUT}/V_{IN}$ , and average inductor current are equal to the output current.


Since the average output current cannot exceed the device's rated output, the available load current is reduced by a factor of  $1 - D$ . So for this design, the maximum available DC load current is  $I_{SW} \times (1 - D) = I_{Load}$ , where  $I_{SW}$  is the average rated current of the high-side switch FET.

In addition, the inductor AC ripple current should be kept small for several reasons. The peak inductor current, which is the average inductor current plus half the peak-to-peak AC current, must be below the internal circuit's current limit. The inductor AC ripple current also determines the DC output current below which the circuit begins to operate in the discontinuous conduction mode. This operation mode occurs when the DC output current is equal to half the peak-to-peak AC current. In general, this restriction will be more severe than the current limit. The ripple current also contributes significantly to the output-voltage ripple. Lower inductor ripple currents provide cleaner output voltages.

For the inverting buck-boost converter, there are significant differences between discontinuous- and continuous-mode operation. Designs that are stable in the discontinuous mode may become unstable when increased load current causes them to operate in the continuous mode, during which the feedback loop contains a right-half-plane zero.<sup>1</sup>

A bypass capacitor from  $V_{IN}$  to ground and from  $V_{IN}$  to  $V_{OUT}$  should be used on the input. The bypass from  $V_{IN}$  to  $V_{OUT}$  is across the device voltage input.

**Figure 2. Inverting buck-boost topology**

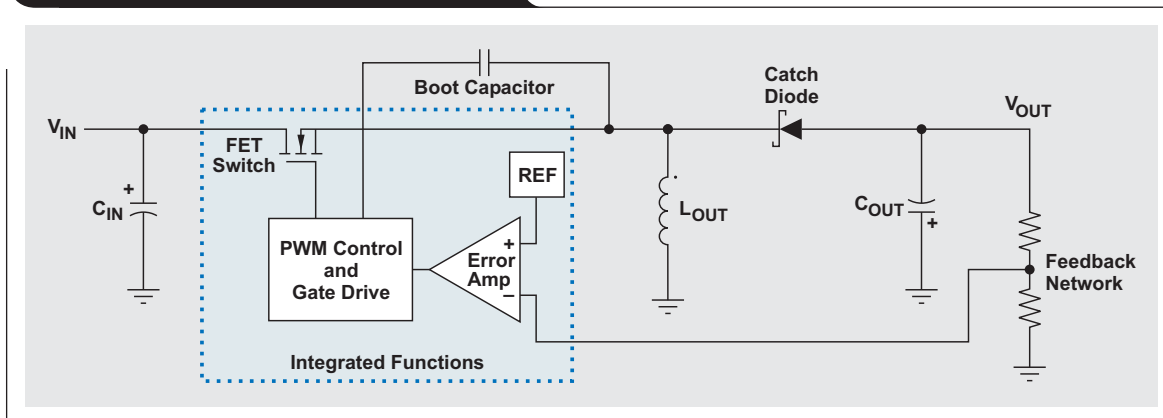


### Typical waveforms

To demonstrate some of the performance differences between the two topologies, a test circuit was constructed for each type. Both circuits use a 24-V input. The buck converter has a 5-V output at 2 A, while the inverting buck-boost converter has a -5-V output, also at 2 A. Output voltage ripple and switching-node waveforms for the inverting buck-boost and buck converters are shown in Figures 3 and 4. Note that the switching-node voltage varies from  $V_{IN}$  to  $V_{OUT}$  for the inverting buck-boost converter, and from  $V_{IN}$  to ground for the buck converter. The ground reference line is indicated by the C2 marker at the left edge of each figure. Also observe that the output voltage ripple does not show the linear ramp characteristic typical of the buck converter. In the buck converter, the average inductor current is delivered to the load while the AC portion is shunted to ground through the output-filter capacitor. The primary component of the ripple voltage is the AC ripple current times the equivalent series resistance of the output cap, resulting in a waveform resembling a ramp that


rises during the FET switch on time and falls during the switch off time. For the inverting buck-boost converter, the output capacitor supplies the load current during the switch on time and is recharged during the switch off time. This charge-and-discharge cycle is superimposed with the AC ripple current to create a more complex ripple current as shown in the figures. Remember that the output voltage is negative, so the positive portions of the waveform represent the output becoming less negative, or the discharge portion of the cycle.

Figures 5 and 6 show the current flowing in the high-side switch for the inverting buck-boost and buck converters, respectively, each with the same load current of 2 A. The positive pulse represents the current flowing through the switch into the inductor during the conduction time. When the switch is off, the inductor current for the inverting buck-boost converter in Figure 5 must remain continuous and flows through the catch diode rather than the high-side switching element. For the buck converter in Figure 6, the average current during conduction is equal to the output


**Figure 3. Inverting buck-boost output voltage ripple and switching-node voltage**

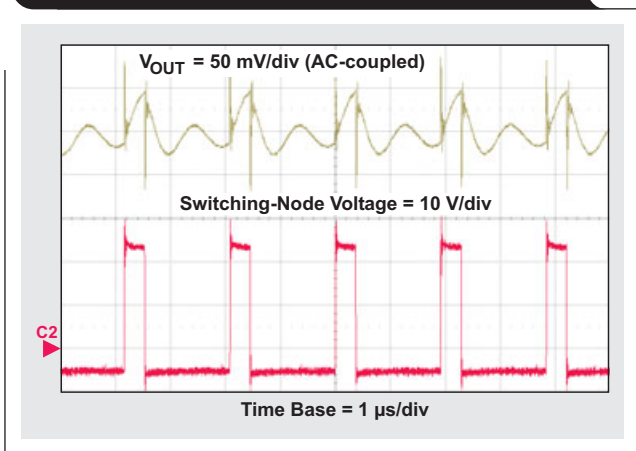


**Figure 5. Inverting buck-boost switch current**

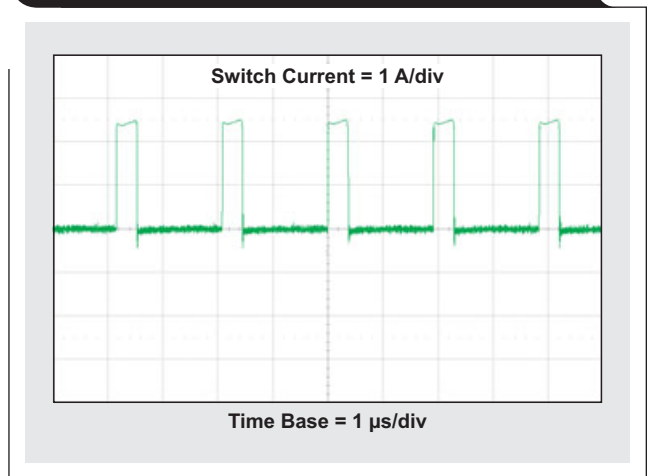

**Figure 4. Buck output voltage ripple and switching-node voltage**

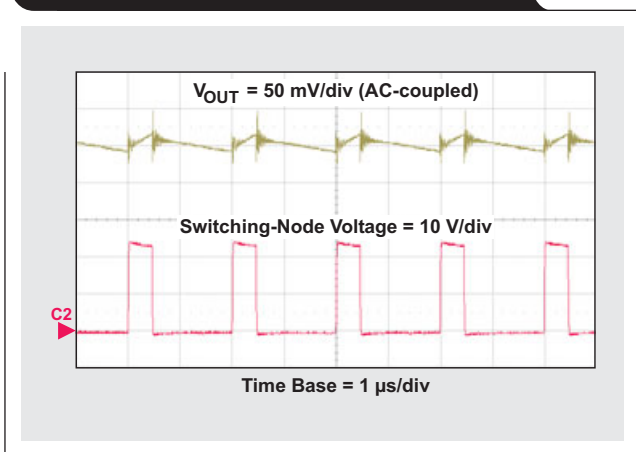

**Figure 6. Buck switch current**

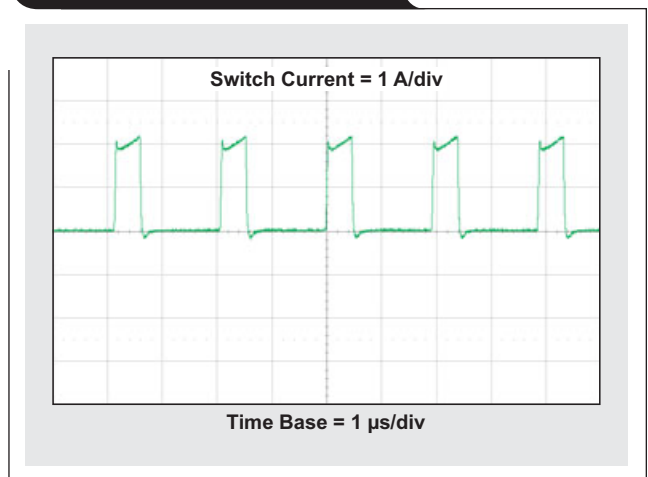

current, as the inductor is connected directly to the output. In this topology the output current is supplied by the inductor during both the on and off times. For the inverting buck-boost converter, this is not the case; so the average switch current during the on time is  $I_{OUT}/(1 - D)$ .

### Input-voltage limitations

In addition to the converter's input-voltage constraint of  $V_{IN} - (-V_{OUT})$ , there may also be a limit to the input voltage at the low end besides that required by any minimum duty cycle or on-time specifications. Many DC/DC converter circuits include an undervoltage lockout (UVLO) circuit. In the buck configuration, the minimum input voltage would be limited by the UVLO level. This limitation exists for the inverting buck-boost converter as well; however, the UVLO threshold is relative to the device ground, which is configured as  $V_{OUT}$ . At start-up, the output is 0 V; so the minimum input voltage to guarantee proper start-up is equal to the UVLO level, regardless of the difference between  $V_{IN}$  and  $V_{OUT}$ .

### Conclusion

A buck converter can be used to generate a negative output voltage from a positive input voltage if the circuit is configured as an inverting buck-boost converter. The circuit design is straightforward, but these important points should be remembered. The output current is less than

the average inductor current by a factor of  $1 - D$ , so the available output current will be less than the device rating. The output voltage is negative and is available at the device ground pin, so the effective voltage across the input of the device is  $V_{IN} - V_{OUT}$ . This difference must not exceed the input-voltage rating of the device. Finally, the ground of the device should not be tied to the system ground.

For a detailed design example using this technique, see Reference 2.

### References

For more information related to this article, you can download an Acrobat Reader file at [www-s.ti.com/sc/techlit/litnumber](http://www-s.ti.com/sc/techlit/litnumber) and replace "litnumber" with the **TI Lit. #** for the materials listed below.

Document Title	TI Lit. #
1. "The Right-Half-Plane Zero—A Simplified Explanation" . . . . .	.slup084
2. John Tucker, "Using the TPS5430 as an Inverting Buck-Boost Converter," Application Report . . . . .	.slva257

### Related Web sites

[power.ti.com](http://power.ti.com)

[www.ti.com/sc/device/TPS5430](http://www.ti.com/sc/device/TPS5430)

# Index of Articles

Title	Issue	Page	Lit. No.
<b>Data Acquisition</b>			
Aspects of data acquisition system design	August 1999	1	SLYT191
Low-power data acquisition sub-system using the TI TLV1572	August 1999	4	SLYT192
Evaluating operational amplifiers as input amplifiers for A-to-D converters	August 1999	7	SLYT193
Precision voltage references	November 1999	1	SLYT183
Techniques for sampling high-speed graphics with lower-speed A/D converters	November 1999	5	SLYT184
A methodology of interfacing serial A-to-D converters to DSPs	February 2000	1	SLYT175
The operation of the SAR-ADC based on charge redistribution	February 2000	10	SLYT176
The design and performance of a precision voltage reference circuit for 14-bit and 16-bit A-to-D and D-to-A converters	May 2000	1	SLYT168
Introduction to phase-locked loop system modeling	May 2000	5	SLYT169
New DSP development environment includes data converter plug-ins	August 2000	1	SLYT158
Higher data throughput for DSP analog-to-digital converters	August 2000	5	SLYT159
Efficiently interfacing serial data converters to high-speed DSPs	August 2000	10	SLYT160
Smallest DSP-compatible ADC provides simplest DSP interface	November 2000	1	SLYT148
Hardware auto-identification and software auto-configuration for the TLV320AIC10 DSP Codec — a “plug-and-play” algorithm	November 2000	8	SLYT149
Using quad and octal ADCs in SPI mode	November 2000	15	SLYT150
Building a simple data acquisition system using the TMS320C31 DSP	February 2001	1	SLYT136
Using SPI synchronous communication with data converters — interfacing the MSP430F149 and TLV5616	February 2001	7	SLYT137
A/D and D/A conversion of PC graphics and component video signals, Part 1: Hardware	February 2001	11	SLYT138
A/D and D/A conversion of PC graphics and component video signals, Part 2: Software and control	July 2001	5	SLYT129
Intelligent sensor system maximizes battery life: Interfacing the MSP430F123 Flash MCU, ADS7822, and TPS60311	1Q, 2002	5	SLYT123
SHDSL AFE1230 application	2Q, 2002	5	SLYT114
Synchronizing non-FIFO variations of the THS1206	2Q, 2002	12	SLYT115
Adjusting the A/D voltage reference to provide gain	3Q, 2002	5	SLYT109
MSC1210 debugging strategies for high-precision smart sensors	3Q, 2002	7	SLYT110
Using direct data transfer to maximize data acquisition throughput	3Q, 2002	14	SLYT111
Interfacing op amps and analog-to-digital converters	4Q, 2002	5	SLYT104
ADS82x ADC with non-uniform sampling clock	4Q, 2003	5	SLYT089
Calculating noise figure and third-order intercept in ADCs	4Q, 2003	11	SLYT090
Evaluation criteria for ADSL analog front end	4Q, 2003	16	SLYT091
Two-channel, 500-kSPS operation of the ADS8361	1Q, 2004	5	SLYT082
ADS809 analog-to-digital converter with large input pulse signal	1Q, 2004	8	SLYT083
Streamlining the mixed-signal path with the signal-chain-on-chip MSP430F169	3Q, 2004	5	SLYT078
Supply voltage measurement and ADC PSRR improvement in MSC12xx devices	1Q, 2005	5	SLYT073
14-bit, 125-MSPS ADS5500 evaluation	1Q, 2005	13	SLYT074
Clocking high-speed data converters	1Q, 2005	20	SLYT075
Implementation of 12-bit delta-sigma DAC with MSC12xx controller	1Q, 2005	27	SLYT076
Using resistive touch screens for human/machine interface	3Q, 2005	5	SLYT209A
Simple DSP interface for ADS784x/834x ADCs	3Q, 2005	10	SLYT210
Operating multiple oversampling data converters	4Q, 2005	5	SLYT222
Low-power, high-intercept interface to the ADS5424 14-bit, 105-MSPS converter for undersampling applications	4Q, 2005	10	SLYT223
Understanding and comparing datasheets for high-speed ADCs	1Q, 2006	5	SLYT231
Matching the noise performance of the operational amplifier to the ADC	2Q, 2006	5	SLYT237
Using the ADS8361 with the MSP430 USI port	3Q, 2006	5	SLYT244
Clamp function of high-speed ADC THS1041	4Q, 2006	5	SLYT253
Conversion latency in delta-sigma converters	2Q, 2007	5	SLYT264
Calibration in touch-screen systems	3Q, 2007	5	SLYT277
Using a touch-screen controller’s auxiliary inputs	4Q, 2007	5	SLYT283

Title	Issue	Page	Lit. No.
<b>Power Management</b>			
Stability analysis of low-dropout linear regulators with a PMOS pass element	August 1999	10	SLYT194
Extended output voltage adjustment (0 V to 3.5 V) using the TI TPS5210	August 1999	13	SLYT195
Migrating from the TI TL770x to the TI TLC770x	August 1999	14	SLYT196
TI TPS5602 for powering TI's DSP	November 1999	8	SLYT185
Synchronous buck regulator design using the TI TPS5211 high-frequency hysteretic controller	November 1999	10	SLYT186
Understanding the stable range of equivalent series resistance of an LDO regulator	November 1999	14	SLYT187
Power supply solutions for TI DSPs using synchronous buck converters	February 2000	12	SLYT177
Powering Celeron-type microprocessors using TI's TPS5210 and TPS5211 controllers	February 2000	20	SLYT178
Simple design of an ultra-low-ripple DC/DC boost converter with TPS60100 charge pump	May 2000	11	SLYT170
Low-cost, minimum-size solution for powering future-generation Celeron™-type processors with peak currents up to 26 A	May 2000	14	SLYT171
Advantages of using PMOS-type low-dropout linear regulators in battery applications	August 2000	16	SLYT161
Optimal output filter design for microprocessor or DSP power supply	August 2000	22	SLYT162
Understanding the load-transient response of LDOs	November 2000	19	SLYT151
Comparison of different power supplies for portable DSP solutions working from a single-cell battery	November 2000	24	SLYT152
Optimal design for an interleaved synchronous buck converter under high-slew-rate, load-current transient conditions	February 2001	15	SLYT139
–48-V/+48-V hot-swap applications	February 2001	20	SLYT140
Power supply solution for DDR bus termination	July 2001	9	SLYT130
Runtime power control for DSPs using the TPS62000 buck converter	July 2001	15	SLYT131
Power control design key to realizing InfiniBand™ benefits	1Q, 2002	10	SLYT124
Comparing magnetic and piezoelectric transformer approaches in CCFL applications	1Q, 2002	12	SLYT125
Why use a wall adapter for ac input power?	1Q, 2002	18	SLYT126
SWIFT™ Designer power supply design program	2Q, 2002	15	SLYT116
Optimizing the switching frequency of ADSL power supplies	2Q, 2002	23	SLYT117
Powering electronics from the USB port	2Q, 2002	28	SLYT118
Using the UCC3580-1 controller for highly efficient 3.3-V/100-W isolated supply design	4Q, 2002	8	SLYT105
Power conservation options with dynamic voltage scaling in portable DSP designs	4Q, 2002	12	SLYT106
Understanding piezoelectric transformers in CCFL backlight applications	4Q, 2002	18	SLYT107
Load-sharing techniques: Paralleling power modules with overcurrent protection	1Q, 2003	5	SLYT100
Using the TPS61042 white-light LED driver as a boost converter	1Q, 2003	7	SLYT101
Auto-Track™ voltage sequencing simplifies simultaneous power-up and power-down	3Q, 2003	5	SLYT095
Soft-start circuits for LDO linear regulators	3Q, 2003	10	SLYT096
UCC28517 100-W PFC power converter with 12-V, 8-W bias supply, Part 1	3Q, 2003	13	SLYT097
UCC28517 100-W PFC power converter with 12-V, 8-W bias supply, Part 2	4Q, 2003	21	SLYT092
LED-driver considerations	1Q, 2004	14	SLYT084
Tips for successful power-up of today's high-performance FPGAs	3Q, 2004	11	SLYT079
A better bootstrap/bias supply circuit	1Q, 2005	33	SLYT077
Understanding noise in linear regulators	2Q, 2005	5	SLYT201
Understanding power supply ripple rejection in linear regulators	2Q, 2005	8	SLYT202
Miniature solutions for voltage isolation	3Q, 2005	13	SLYT211
New power modules improve surface-mount manufacturability	3Q, 2005	18	SLYT212
Li-ion switching charger integrates power FETs	4Q, 2005	19	SLYT224
TLC5940 dot correction compensates for variations in LED brightness	4Q, 2005	21	SLYT225
Powering today's multi-rail FPGAs and DSPs, Part 1	1Q, 2006	9	SLYT232
TPS79918 RF LDO supports migration to StrataFlash® Embedded Memory (P30)	1Q, 2006	14	SLYT233
Practical considerations when designing a power supply with the TPS6211x	1Q, 2006	17	SLYT234
TLC5940 PWM dimming provides superior color quality in LED video displays	2Q, 2006	10	SLYT238
Wide-input dc/dc modules offer maximum design flexibility	2Q, 2006	13	SLYT239
Powering today's multi-rail FPGAs and DSPs, Part 2	2Q, 2006	18	SLYT240
TPS61059 powers white-light LED as photoflash or movie light	3Q, 2006	8	SLYT245
TPS65552A powers portable photoflash	3Q, 2006	10	SLYT246
Single-chip bq2403x power-path manager charges battery while powering system	3Q, 2006	12	SLYT247
Complete battery-pack design for one- or two-cell portable applications	3Q, 2006	14	SLYT248
A 3-A, 1.2-V <sub>OUT</sub> linear regulator with 80% efficiency and P <sub>LOST</sub> < 1 W	4Q, 2006	10	SLYT254

Title	Issue	Page	Lit. No.
<b>Power Management (Continued)</b>			
bq25012 single-chip, Li-ion charger and dc/dc converter for Bluetooth® headsets	4Q, 2006	13	SLYT255
Fully integrated TPS6300x buck-boost converter extends Li-ion battery life	4Q, 2006	15	SLYT256
Selecting the correct IC for power-supply applications	1Q, 2007	5	SLYT259
LDO white-LED driver TPS7510x provides incredibly small solution size	1Q, 2007	9	SLYT260
Power management for processor core voltage requirements	1Q, 2007	11	SLYT261
Enhanced-safety, linear Li-ion battery charger with thermal regulation and input overvoltage protection	2Q, 2007	8	SLYT269
Current balancing in four-pair, high-power PoE applications	2Q, 2007	11	SLYT270
Power-management solutions for telecom systems improve performance, cost, and size	3Q, 2007	10	SLYT278
TPS6108x: A boost converter with extreme versatility	3Q, 2007	14	SLYT279
Get low-noise, low-ripple, high-PSRR power with the TPS717xx	3Q, 2007	17	SLYT280
Simultaneous power-down sequencing with the TPS74x01 family of linear regulators	3Q, 2007	20	SLYT281
Driving a WLED does not always require 4 V	4Q, 2007	9	SLYT284
Host-side gas-gauge-system design considerations for single-cell handheld applications	4Q, 2007	12	SLYT285
Using a buck converter in an inverting buck-boost topology	4Q, 2007	16	SLYT286
<b>Interface (Data Transmission)</b>			
TIA/EIA-568A Category 5 cables in low-voltage differential signaling (LVDS)	August 1999	16	SLYT197
Keep an eye on the LVDS input levels	November 1999	17	SLYT188
Skew definition and jitter analysis	February 2000	29	SLYT179
LVDS receivers solve problems in non-LVDS applications	February 2000	33	SLYT180
LVDS: The ribbon cable connection	May 2000	19	SLYT172
Performance of LVDS with different cables	August 2000	30	SLYT163
A statistical survey of common-mode noise	November 2000	30	SLYT153
The Active Fail-Safe feature of the SN65LVDS32A	November 2000	35	SLYT154
The SN65LVDS33/34 as an ECL-to-LVTTL converter	July 2001	19	SLYT132
Power consumption of LVPECL and LVDS	1Q, 2002	23	SLYT127
Estimating available application power for Power-over-Ethernet applications	1Q, 2004	18	SLYT085
The RS-485 unit load and maximum number of bus connections	1Q, 2004	21	SLYT086
Failsafe in RS-485 data buses	3Q, 2004	16	SLYT080
Maximizing signal integrity with M-LVDS backplanes	2Q, 2005	11	SLYT203
Device spacing on RS-485 buses	2Q, 2006	25	SLYT241
Improved CAN network security with TI's SN65HVD1050 transceiver	3Q, 2006	17	SLYT249
Detection of RS-485 signal loss	4Q, 2006	18	SLYT257
Enabling high-speed USB OTG functionality on TI DSPs	2Q, 2007	18	SLYT271
<b>Amplifiers: Audio</b>			
Reducing the output filter of a Class-D amplifier	August 1999	19	SLYT198
Power supply decoupling and audio signal filtering for the Class-D audio power amplifier	August 1999	24	SLYT199
PCB layout for the TPA005D1x and TPA032D0x Class-D APAs	February 2000	39	SLYT182
An audio circuit collection, Part 1	November 2000	39	SLYT155
1.6- to 3.6-volt BTL speaker driver reference design	February 2001	23	SLYT141
Notebook computer upgrade path for audio power amplifiers	February 2001	27	SLYT142
An audio circuit collection, Part 2	February 2001	41	SLYT145
An audio circuit collection, Part 3	July 2001	34	SLYT134
Audio power amplifier measurements	July 2001	40	SLYT135
Audio power amplifier measurements, Part 2	1Q, 2002	26	SLYT128

Title	Issue	Page	Lit. No.
<b>Amplifiers: Op Amps</b>			
Single-supply op amp design	November 1999	20	SLYT189
Reducing crosstalk of an op amp on a PCB	November 1999	23	SLYT190
Matching operational amplifier bandwidth with applications	February 2000	36	SLYT181
Sensor to ADC — analog interface design	May 2000	22	SLYT173
Using a decompensated op amp for improved performance	May 2000	26	SLYT174
Design of op amp sine wave oscillators	August 2000	33	SLYT164
Fully differential amplifiers	August 2000	38	SLYT165
The PCB is a component of op amp design	August 2000	42	SLYT166
Reducing PCB design costs: From schematic capture to PCB layout	August 2000	48	SLYT167
Thermistor temperature transducer-to-ADC application	November 2000	44	SLYT156
Analysis of fully differential amplifiers	November 2000	48	SLYT157
Fully differential amplifiers applications: Line termination, driving high-speed ADCs, and differential transmission lines	February 2001	32	SLYT143
Pressure transducer-to-ADC application	February 2001	38	SLYT144
Frequency response errors in voltage feedback op amps	February 2001	48	SLYT146
Designing for low distortion with high-speed op amps	July 2001	25	SLYT133
Fully differential amplifier design in high-speed data acquisition systems	2Q, 2002	35	SLYT119
Worst-case design of op amp circuits	2Q, 2002	42	SLYT120
Using high-speed op amps for high-performance RF design, Part 1	2Q, 2002	46	SLYT121
Using high-speed op amps for high-performance RF design, Part 2	3Q, 2002	21	SLYT112
FilterPro™ low-pass design tool	3Q, 2002	24	SLYT113
Active output impedance for ADSL line drivers	4Q, 2002	24	SLYT108
RF and IF amplifiers with op amps	1Q, 2003	9	SLYT102
Analyzing feedback loops containing secondary amplifiers	1Q, 2003	14	SLYT103
Video switcher using high-speed op amps	3Q, 2003	20	SLYT098
Expanding the usability of current-feedback amplifiers	3Q, 2003	23	SLYT099
Calculating noise figure in op amps	4Q, 2003	31	SLYT094
Op amp stability and input capacitance	1Q, 2004	24	SLYT087
Integrated logarithmic amplifiers for industrial applications	1Q, 2004	28	SLYT088
Active filters using current-feedback amplifiers	3Q, 2004	21	SLYT081
Auto-zero amplifiers ease the design of high-precision circuits	2Q, 2005	19	SLYT204
So many amplifiers to choose from: Matching amplifiers to applications	3Q, 2005	24	SLYT213
Instrumentation amplifiers find your needle in the haystack	4Q, 2005	25	SLYT226
High-speed notch filters	1Q, 2006	19	SLYT235
Low-cost current-shunt monitor IC revives moving-coil meter design	2Q, 2006	27	SLYT242
Accurately measuring ADC driving-circuit settling time	1Q, 2007	14	SLYT262
New zero-drift amplifier has an $I_Q$ of 17 $\mu$ A	2Q, 2007	22	SLYT272
<b>General Interest</b>			
Synthesis and characterization of nickel manganite from different carboxylate precursors for thermistor sensors	February 2001	52	SLYT147
Analog design tools	2Q, 2002	50	SLYT122
Spreadsheet modeling tool helps analyze power- and ground-plane voltage drops to keep core voltages within tolerance	2Q, 2007	29	SLYT273

## TI Worldwide Technical Support

### Internet

#### TI Semiconductor Product Information Center Home Page

support.ti.com

#### TI Semiconductor KnowledgeBase Home Page

support.ti.com/sc/knowledgebase

### Product Information Centers

#### Americas

Phone +1(972) 644-5580  
 Fax +1(972) 927-6377  
 Internet/Email support.ti.com/sc/pic/americas.htm

#### Europe, Middle East, and Africa

Phone  
 European Free Call 00800-ASK-TEXAS (00800 275 83927)  
 International +49 (0) 8161 80 2121  
 Russian Support +7 (4) 95 98 10 701

**Note:** The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax +(49) (0) 8161 80 2045  
 Internet support.ti.com/sc/pic/euro.htm

#### Japan

Fax International +81-3-3344-5317  
 Domestic 0120-81-0036  
 Internet/Email International support.ti.com/sc/pic/japan.htm  
 Domestic www.tij.co.jp/pic

#### Asia

Phone  
 International +886-2-23786800  
 Domestic Toll-Free Number  
 Australia 1-800-999-084  
 China 800-820-8682  
 Hong Kong 800-96-5941  
 India +91-80-41381665 (Toll)  
 Indonesia 001-803-8861-1006  
 Korea 080-551-2804  
 Malaysia 1-800-80-3973  
 New Zealand 0800-446-934  
 Philippines 1-800-765-7404  
 Singapore 800-886-1028  
 Taiwan 0800-006800  
 Thailand 001-800-886-0010  
 Fax +886-2-2378-6808  
 Email tiasia@ti.com or ti-china@ti.com  
 Internet support.ti.com/sc/pic/asia.htm

**Important Notice:** The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A062907

Auto-Track, FilterPro, Impedance Track and SWIFT are trademarks of Texas Instruments. The Bluetooth word mark and logos are owned by the Bluetooth SIG, Inc., and any use of such marks by Texas Instruments is under license. Celeron is a trademark and StrataFlash is a registered trademark of Intel Corporation. InfiniBand is a service mark of the InfiniBand Trade Association. All other trademarks are the property of their respective owners.

SLYT282