

## EVALUATION AND DESIGN SUPPORT

### Circuit Evaluation Boards

[AD7091R Evaluation Board \(EVAL-AD7091RSDZ\)](#)

[System Demonstration Platform \(EVAL-SDP-CB1Z\)](#)

### Design and Integration Files

[Schematics, Layout Files, Bill of Materials](#)

## CIRCUIT FUNCTION AND BENEFITS

The circuit shown in Figure 1 is an ultralow power data acquisition system using the [AD7091R](#) 12-bit, 1 MSPS SAR ADC and an [AD8031](#) op amp driver with a total circuit power dissipation of less than 5 mW on a single 3 V supply.

The low power consumption and small package size of the selected components makes this combination an industry-leading solution for portable battery-operated systems where power dissipation, cost, and size play a critical role.

The [AD7091R](#) requires typically only 350  $\mu\text{A}$  of supply current on the  $V_{\text{DD}}$  pin at 3 V, which is significantly lower than any competitive ADC offering currently available in the market. This translates to  $\sim 1$  mW typical power dissipation.

The [AD8031](#) requires only 800  $\mu\text{A}$  of supply current, that results in 2.4 mW typical power dissipation at 3 V supply, making the total power dissipation of the system less than 5 mW when sampling at 1 MSPS with a 10 kHz analog input signal.

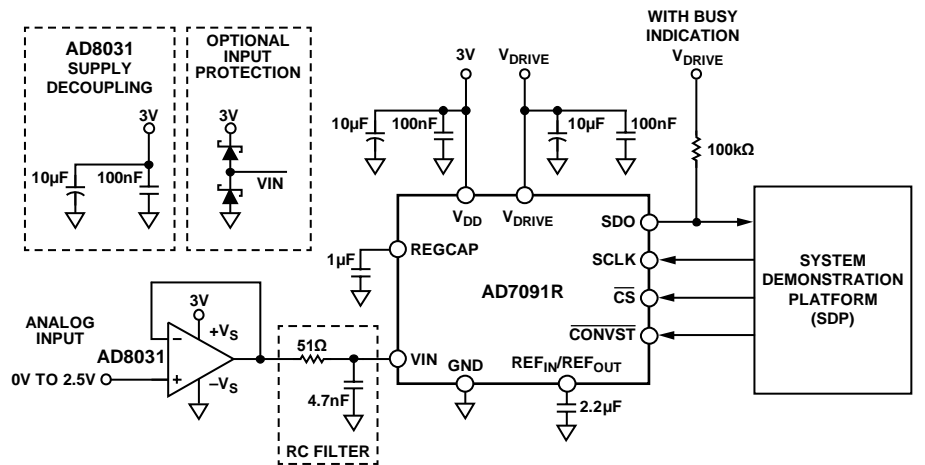


Figure 1. 12-Bit, 1 MSPS Low Power ADC with Driver (Simplified Schematic: All Connections Not Shown)

## CIRCUIT DESCRIPTION

To maximize performance, most SAR ADCs require a suitable input buffer for the analog signal. The buffer isolates the source from the transients generated on the ADC input when the internal track-and-hold switch goes from hold to track. The buffer driving the ADC must recover from this transient and settle to the required accuracy within the acquisition time of the ADC. This is particularly important in applications where the signal source has high source impedance and where low distortion and a high signal-to-noise ratio is important. Selecting the proper buffer op amp is therefore a critical part of the design process.

The [AD7091R](#) is a 12-bit, fast, ultralow power, single-supply ADC with an internal 2.5 V reference. The part can be operated from a 2.7 V to 5.25 V supply. The [AD7091R](#) is capable of throughput rates of 1 MSPS. At a sampling rate of 1 MSPS, the total power dissipation of the [AD7091R](#) with a 10 kHz input signal is approximately 2.3 mW.

This power figure can be reduced in applications where 1 MSPS sampling frequency is not necessary because the [AD7091R](#) power scales with the throughput, as shown in Table 1.

To further reduce power dissipation of the system, reduce the throughput rate of the converter. Table 1 shows the typical power vs. throughput for the [AD7091R](#) at 3 V when operating in normal mode.

Table 1 shows the reduction in power consumption that is achievable when power-down mode is activated. The power-down mode is an extremely useful method to significantly reduce power supply requirements when operating the [AD7091R](#) at lower throughput rates.

The [AD7091R](#) is housed in a tiny, 3 mm × 2 mm, 10-lead LFCSP or a 3 mm × 5 mm, 10-lead MSOP. Both packages offer considerable space saving advantages over competitive solutions.

The [AD8031](#) is a rail-to-rail input/output low power operational amplifier and is an optimum drive amplifier for the [AD7091R](#). The [AD8031](#) can operate from a 2.7 V to 12 V supply, which allows both ICs to be driven from the same supply rail. The [AD8031](#) has an 80 MHz bandwidth, a 30 V/μs slew rate, and a 125 ns settling time to 0.1%.

When operating on a single supply, the output of the [AD8031](#) can go to within 20 mV of the negative rail. If linearity to 0 V

input is needed, the [AD8031](#) requires an additional negative supply (see [Tutorial MT-035](#)).

Figure 1 shows the simplified schematic for the circuit. Well decouple the IC power supply pins to ground using 100 nF and 10 μF ceramic capacitors. Position these capacitors as close as possible to the supply pins of both ICs.

Take care to ensure that the analog input signal to the ADC does not exceed the supply rails by more than 300 mV. If the signal does exceed this level, the internal ESD protection diodes become forward-biased and start conducting current into the substrate. A diode can conduct a maximum current of 10 mA without causing irreversible damage to the part. This can be prevented by connecting a pair of Schottky diodes between VIN and the supply rails of the [AD7091R](#), as described in [Tutorial MT-036](#).

The [AD7091R](#) contains an internal 2.5 V reference. Well decouple the REF<sub>IN</sub>/REF<sub>OUT</sub> pin to achieve the specified performance. The typical value for the REF<sub>IN</sub>/REF<sub>OUT</sub> capacitor is 2.2 μF. Note that the internal reference voltage can be overdriven externally.

If an external reference voltage is used, the range must be between 2.7 V to V<sub>DD</sub>, and it must be connected to the REF<sub>IN</sub>/REF<sub>OUT</sub> pin. A typical value for the regulator bypass (REGCAP) decoupling capacitor is 1 μF.

The voltage applied to the V<sub>DRIVE</sub> input controls the logic level voltage of the serial interface. Connect this pin to the supply voltage of the logic family connected to the [AD7091R](#) digital outputs. V<sub>DRIVE</sub> can be set in the 1.8 V to V<sub>DD</sub> range. Typical values for the V<sub>DRIVE</sub> decoupling capacitors are 100 nF in parallel with 10 μF.

If the busy indication function is required, connect a pull-up resistor of 100 kΩ between the V<sub>DRIVE</sub> and the SDO pin.

The [AD8031](#) that is used to buffer analog input of the [AD7091R](#) is configured as a unity gain buffer. A single-pole RC filter follows the op amp output stage to reduce out-of-band noise. The cutoff frequency of the RC filter is set to 660 kHz. However, depending on the system throughput rate specification, this parameter can vary. In systems where the [AD7091R](#) is not operated at maximum throughput rate, the filter cutoff frequency can be reduced. Depending on the analog signal input amplitude and offset, the [AD8031](#) operational amplifier can be configured to provide gain, attenuation, and level shifting, to match the input signal swing to the analog input range of the ADC.

**Table 1. Typical Power vs. Throughput for the [AD7091R](#) at 3 V when Operating in Normal Mode**

Mode	I <sub>DD</sub>	I <sub>DRIVE</sub>	I <sub>AMP</sub> (μA)	Total Current (μA)	Total Power (mW)
Power Down	550 nA	36 nA	766	767	2.3
Static (Power On, Input Grounded, No Clock)	21 μA	81 nA	766	787	2.4
Operating (Power On, 10 kHz Input, 1 MSPS Sampling)	368 μA	406 μA	766	1540	4.6
Operating (Power On, Input Grounded, 1 MSPS Sampling)	344 μA	35 μA	766	1145	3.4
Operating (Power On, Input Grounded, 1 kSPS Sampling)	57.8 μA	18.9 μA	766	843	2.5

Note that convert start pulse width = 20 ns when sampling, V<sub>DD</sub> = V<sub>DRIVE</sub> = 3 V.

Figure 2 and Figure 3 show the integral nonlinearity (INL) and differential nonlinearity (DNL) plots for the circuit. Note that the INL and DNL is less than  $\pm 1$  LSB.

 


Figure 2. INL for Sampling Rate of 1 MSPS

 


Figure 3. DNL for Sampling Rate of 1 MSPS

Figure 4 displays the FFT data calculated for 8192 samples captured at the 1 MSPS rate with an analog input frequency of 10 kHz. The SNR is 70.44 dBFS.

 


Figure 4. FFT of System, Input = 10 kHz, Sampling Frequency = 1 MSPS

The circuit must be constructed on a multilayer printed circuit board (PCB) with a large area ground plane. Proper layout, grounding, and decoupling techniques must be used to achieve optimum performance (see [Tutorial MT-031](#), [Tutorial MT-101](#), and the [AD7091R](#) evaluation board layout shown in the [CN-0247 Design Support Package](#)).

Values of the components surrounding the [AD7091R](#) and the [AD8031](#) can be modified to meet specific requirements of the application and sensor. For example, the buffer can be configured to provide gain and offset, and the cutoff frequency of the RC filter can be changed depending on the sampling frequency and input frequency.

A complete documentation package including schematics, board layout, and bill of materials (BOM) can be found at <http://www.analog.com/CN0247-DesignSupport>.

### COMMON VARIATIONS

The AD7091 is similar to the [AD7091R](#) and is available in an 8-lead 2 mm  $\times$  2 mm LFCSP. The AD7091 uses the  $V_{DD}$  supply as a reference and does not contain an internal one.

## CIRCUIT EVALUATION AND TEST

The EVAL-AD7091RSDZ evaluation board is developed to evaluate and test the AD7091R device with the circuitry described in this circuit note. A detailed schematic and user instructions are available in the EVAL-AD7091RSDZ documentation. A functional block diagram of the test setup is shown in Figure 5.

### Equipment Needed

The following equipment is required to test the circuit:

- EVAL-AD7091RSDZ Evaluation Board (includes software and 9 V dc wall wart power supply)
- EVAL-SDP-CB1Z System Demonstration Platform Board
- A low distortion signal generator, such as the Agilent 81150A or Audio Precision System Two 2322
- A PC with an USB 2.0 Port running Windows® XP, Windows Vista, or Windows 7 (32-Bit or 64-bit)
- Power supplies: 9 V dc wall wart (included with evaluation board, external 3 V dc supply at 50 mA)

### Setup

Before connecting any hardware, ensure that the links on the EVAL-AD7091RSDZ evaluation board are positioned as follows:

- LK1: Position A (selects the AD8031 as the input buffer)
- LK2: Position A (connects the input at J5 to the input buffer)
- LK5: Position A (enables external V<sub>DRIVE</sub> source)
- LK6: Position B (enables external V<sub>DD</sub> source)

From this point, follow the evaluation board documentation to connect the hardware and install the software.

### Test

Refer to the evaluation board documentation for the complete description on how to run the various tests contained in this circuit note.

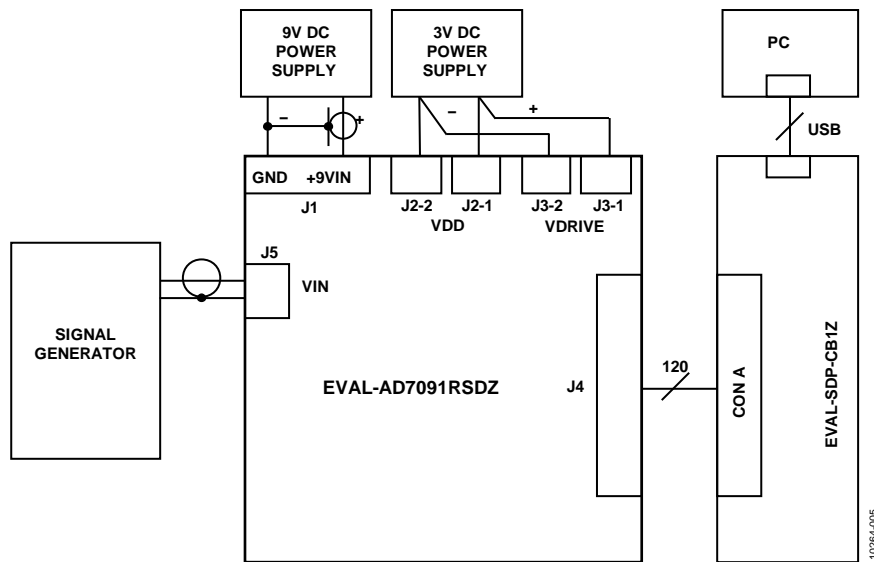


Figure 5. Functional Diagram of Test Setup

## LEARN MORE

CN-0247 Design Support Package:

<http://www.analog.com/CN0247-DesignSupport>

MT-031 Tutorial, *Grounding Data Converters and Solving the Mystery of "AGND" and "DGND"*, Analog Devices.

MT-035 Tutorial, *Op Amp Inputs, Outputs, Single-Supply, and Rail-to-Rail Issues*, Analog Devices.

MT-036 Tutorial, *Op Amp Output Phase-Reversal and Input Over-Voltage Protection*, Analog Devices.

MT-101 Tutorial, *Decoupling Techniques*, Analog Devices.

## Data Sheets and Evaluation Boards

[AD7091R data sheet and evaluation board](#)

[System Demonstration Platform \(EVAL-SDP-CB1Z\)](#)

[AD8031 Data Sheet](#)

## REVISION HISTORY

4/12—Revision 0: Initial Version

(Continued from first page) Circuits from the Lab circuits are intended only for use with Analog Devices products and are the intellectual property of Analog Devices or its licensors. While you may use the Circuits from the Lab circuits in the design of your product, no other license is granted by implication or otherwise under any patents or other intellectual property by application or use of the Circuits from the Lab circuits. Information furnished by Analog Devices is believed to be accurate and reliable. However, Circuits from the Lab circuits are supplied "as is" and without warranties of any kind, express, implied, or statutory including, but not limited to, any implied warranty of merchantability, noninfringement or fitness for a particular purpose and no responsibility is assumed by Analog Devices for their use, nor for any infringements of patents or other rights of third parties that may result from their use. Analog Devices reserves the right to change any Circuits from the Lab circuits at any time without notice but is under no obligation to do so.

©2012 Analog Devices, Inc. All rights reserved. Trademarks and registered trademarks are the property of their respective owners.  
CN10264-0-4/12(0)

