

**Circuits from the Lab™**  
Reference Circuits

*Circuits from the Lab™ reference circuits are engineered and tested for quick and easy system integration to help solve today's analog, mixed-signal, and RF design challenges. For more information and/or support, visit [www.analog.com/CN0260](http://www.analog.com/CN0260).*

### Devices Connected/Referenced

<a href="#">AD7985</a>	16-Bit, 2.5 MSPS, 15.5 mW PuSAR® ADC in LFCSP
<a href="#">AD8253</a>	10 MHz, 20 V/μs, G = 1, 10, 100, 1000 iCMOS® Programmable Gain Instrumentation Amplifier
<a href="#">AD8021</a>	Low Noise, High Speed Amplifier for 16-Bit Systems
<a href="#">ADA4004-2</a>	1.8 nV/√Hz, 36 V Precision Dual Amplifier
<a href="#">ADR439</a>	Ultralow Noise, 4.5 V XFET® Voltage Reference with Current Sink and Source Capability

## Oversampled SAR ADC with PGA Achieving Greater Than 125 dB Dynamic Range

### EVALUATION AND DESIGN SUPPORT

#### Design and Integration Files

[Schematics](#), [Layout Files](#), [Bill of Materials](#)

### CIRCUIT FUNCTION AND BENEFITS

This circuit, shown in Figure 1, is a flexible sensor signal conditioning block, with low noise, relatively high gain, and the ability to dynamically change the gain in response to input level changes without affecting performance, while still maintaining a wide dynamic range. Existing sigma-delta technology can

provide the dynamic range needed for many applications, but only at the expense of low update rates. This circuit presents an alternative approach that uses the [AD7985](#) 16-bit, 2.5 MSPS PuSAR® successive-approximation ADC, combined with an autoranging [AD8253](#) iCMOS® programmable gain instrumentation amplifier (PGA) front end. With gain that changes automatically based on analog input value, it uses oversampling and digital processing to increase the dynamic range of the system to more than 125 dB.

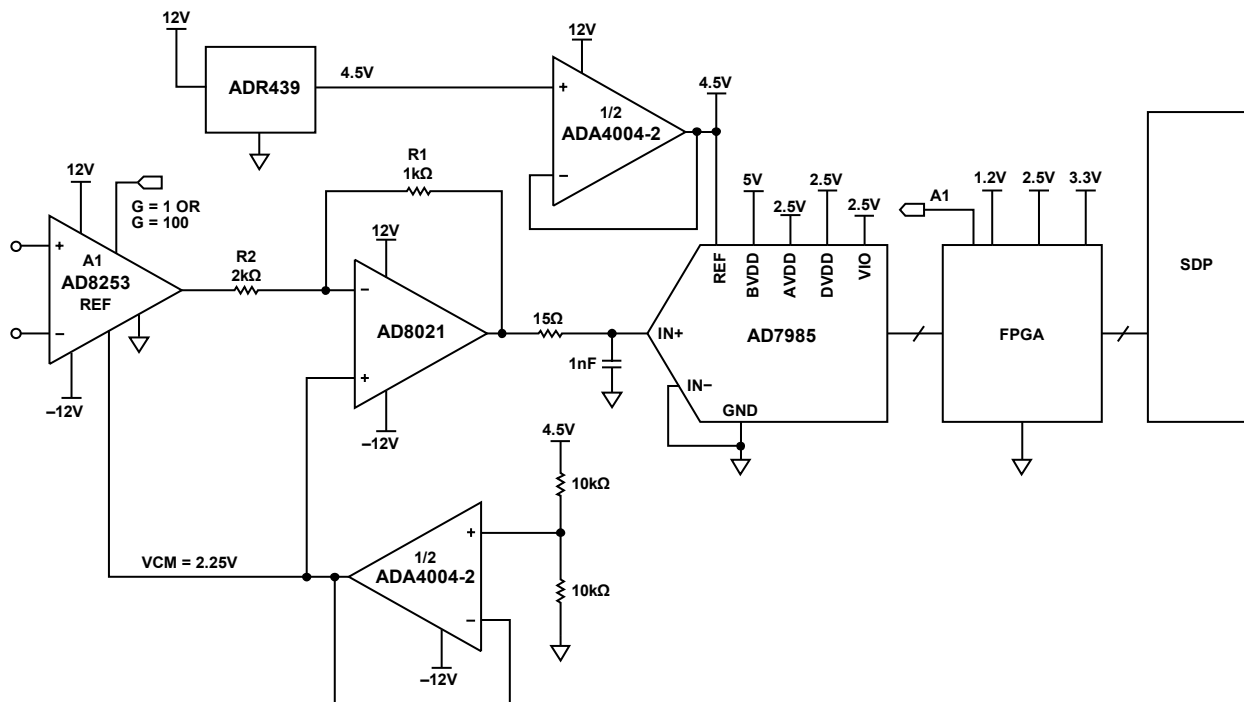


Figure 1. Wide Dynamic Range Signal Conditioning Circuit with Autoranging PGA and Oversampling SAR ADC (Note: All Connections and Decoupling Not Shown)

#### Rev.0

Circuits from the Lab™ circuits from Analog Devices have been designed and built by Analog Devices engineers. Standard engineering practices have been employed in the design and construction of each circuit, and their function and performance have been tested and verified in a lab environment at room temperature. However, you are solely responsible for testing the circuit and determining its suitability and applicability for your use and application. Accordingly, in no event shall Analog Devices be liable for direct, indirect, special, incidental, consequential or punitive damages due to any cause whatsoever connected to the use of any Circuits from the Lab circuits. (Continued on last page)

One Technology Way, P.O. Box 9106, Norwood, MA 02062-9106, U.S.A.  
Tel: 781.329.4700 [www.analog.com](http://www.analog.com)  
Fax: 781.461.3113 ©2012 Analog Devices, Inc. All rights reserved.

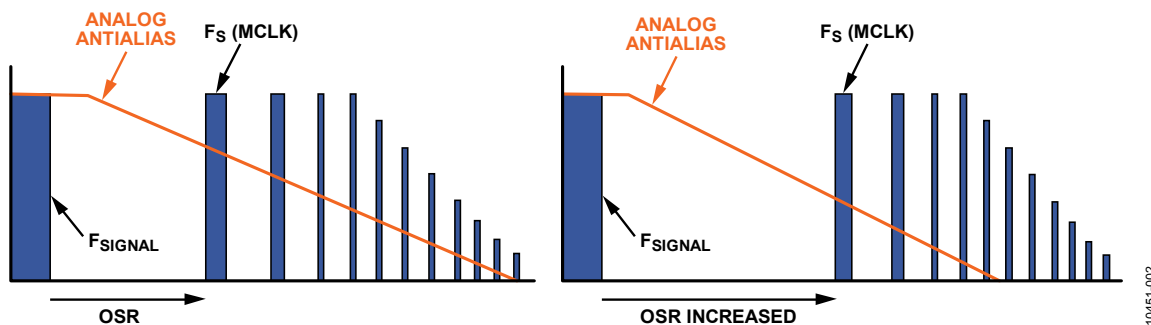


Figure 2. Increasing Oversampling Ratio (OSR) Reduces Noise

## CIRCUIT DESCRIPTION

There are many applications that require wide dynamic range. Weigh scale systems typically use load cell bridge sensors with maximum full-scale outputs of 1 mV to 2 mV. Such systems may require resolutions on the order of 1,000,000 to 1, which, when referred to a 2 mV full-scale input, call for a high performance, low noise, high gain amplifier and a sigma-delta modulator. Similarly, chemical and blood analyses for medical applications often use photodiode sensors, producing very small currents that need to be accurately measured. Some applications, such as vibration monitoring systems, contain both ac and dc information, so the ability to accurately monitor both small and large signals is growing in importance. Sigma-delta ADCs implement this well in many cases but are limited when both ac and dc measurements are needed and fast gain switching is required.

Oversampling is the process of sampling the input signal at a much higher rate than the Nyquist frequency. As a general rule, every doubling of the sampling frequency yields approximately a 3 dB improvement in noise performance within the original signal bandwidth. The oversampling ADC is followed by digital postprocessing to remove the noise outside the signal bandwidth, as shown in Figure 2.

To achieve maximum dynamic range, a front-end PGA stage can be added to increase the effective signal-to-noise ratio (SNR) for very small signal inputs. Consider a system dynamic range requirement of >126 dB. First, calculate the minimum rms noise required to achieve this dynamic range. For example, a 3 V input range (6 V p-p) has a 2.12 V full-scale rms value ( $6/2\sqrt{2}$ ). The maximum allowable system noise is calculated as

$$126 \text{ dB} = 20 \log (2.12 \text{ V/rms noise})$$

Thus, the rms noise  $\approx 1 \mu\text{V}$  rms.

Now, consider the system update rate, which will determine the oversampling ratio and the maximum amount of noise, referred to the input (RTI), that can be tolerated in the system. For example, with the [AD7985](#) 16-bit, 2.5 MSPS PulSAR ADC

running at 600 kSPS (11 mW dissipation) and an oversampling ratio of 72, the effective throughput rate of the system after averaging and decimation is  $600 \text{ kSPS} \div 72 = 8.33 \text{ kSPS}$ . The input signal is therefore limited to a bandwidth of approximately 4 kHz.

The total rms noise is simply the noise density (ND) times  $\sqrt{f}$ , so the maximum allowable input spectral noise density (ND) can be calculated as

$$1 \mu\text{V rms} = \text{ND} \times \sqrt{4 \text{ kHz}}$$

Or,  $\text{ND} = 15.8 \text{ nV}/\sqrt{\text{Hz}}$ .

From this figure of merit for RTI system input noise, a suitable instrumentation amplifier can be chosen that will provide sufficient analog front-end gain (when summed with the SNR of the ADC, with associated oversampling) to achieve the required 126 dB. For the [AD7985](#), the typical SNR figure is 89 dB, and oversampling by 72 yields another  $\sim 18$  dB improvement (72 is approximately  $2^6$ , and each doubling adds 3 dB). Achieving 126 dB DR still requires more than 20 dB improvement, which can come from the gain provided by the analog PGA stage. The instrumentation amplifier must provide a gain of  $\geq 20$  (or whatever will not exceed a noise density specification of  $15.8 \text{ nV}/\sqrt{\text{Hz}}$ ).

A system-level solution to implement front-end PGA gain and ADC oversampling as discussed above is shown in Figure 1. The input stage uses the [AD8253](#) very low noise  $10 \text{ nV}/\sqrt{\text{Hz}}$  digitally controlled instrumentation amplifier. Gain options are the following:  $G = 1, 10, 100, 1000$ .

The [AD8021](#) is a  $2.1 \text{ nV}/\sqrt{\text{Hz}}$  low noise, high speed amplifier capable of driving the [AD7985](#). It also level shifts and attenuates the [AD8253](#) output. Both the [AD8253](#) and [AD8021](#) are operated with an external common-mode bias voltage of 2.25 V, which combine to maintain the same common-mode voltage on the input to the ADC. With a 4.5 V reference, the input range of the ADC is 0 V to 4.5 V.

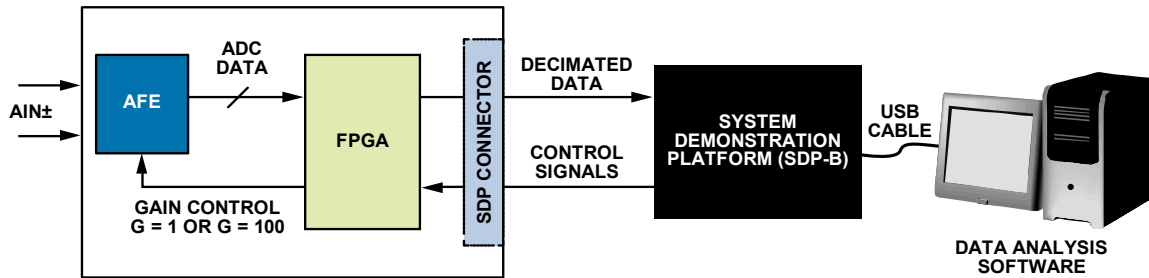


Figure 3. Test Setup Used to Measure Performance of System

The output of the [AD8021](#) is measured using a high speed ADC. The PGA gain can be dynamically set based on the amplitude of the input signal. For small signal inputs, a gain of 100 is programmed. For larger inputs, the gain is reduced to 1.

Digital postprocessing is implemented using the [AD7985](#) 16-bit, 2.5 MSPS PulSAR ADC (11 mW dissipation) in a QFN package, which, by virtue of its fast sampling rates, can also be used to implement high orders of oversampling for low input bandwidth applications. Since the complete system noise budget is 15.8 nV/ $\sqrt{\text{Hz}}$  maximum, referred to the input (RTI), it is useful to calculate the dominant noise sources of each block to ensure that the 15.8 nV/ $\sqrt{\text{Hz}}$  hard limit is not exceeded. The [AD8021](#) has an input-referred noise specification of <3 nV/ $\sqrt{\text{Hz}}$ , which is negligible when referred back to the input of the gain-of-100 [AD8253](#) stage. The [AD7985](#) has a specified SNR of 89 dB, using an external 4.5 V reference, for a noise resolution of <45  $\mu\text{V}$  rms.

Considering the Nyquist bandwidth of 300 kHz for the ADC, it will contribute ~83 nV/ $\sqrt{\text{Hz}}$  across this bandwidth. When referred back to the input of the [AD7985](#), its <1 nV/ $\sqrt{\text{Hz}}$  noise will be negligible in the system, where the RTI noise sources are summed using a root-sum-of-squares calculation.

A further benefit of using the [AD8253](#) is that it has digital gain control, which allows the system gain to be dynamically changed in response to changes in the input. This is achieved by intelligently using the system's digital signal processing capability. The main function of digital processing in this application is to produce a higher resolution output, using the [AD7985](#) 16-bit conversion results. This is achieved by averaging and decimating the data and switching the analog input gain automatically, depending on the input amplitude. The oversampling process results in a lower output data rate than ADC sample rate, but with a greatly increased dynamic range.

To prototype the digital side of this application, a field-programmable gate array (FPGA) was used as the digital core. To rapidly debug the system, the analog circuitry and the FPGA were consolidated onto a single board using the system

demonstration platform (SDP) connector standard to allow easy USB connectivity to the PC, as shown in Figure 3. The SDP is a combination of reusable hardware and software that allows easy control of and data capture from hardware over the most commonly used component interfaces.

This module outputs a new gain setting based on the current gain setting, two raw ADC samples, and some hard-coded threshold figures. Four thresholds are used in the system. The selection of these thresholds is critical to maximizing the analog input range of the system, ensuring the G = 100 mode is used for as much of the signal range as possible, while also preventing the ADC input from being overdriven. Note that this gain block operates on every raw ADC result, not on data that has been normalized. Bearing this in mind, an illustrative example of some thresholds that could be used in a system such as this (assuming a bipolar system with a mid-scale of zero):

- T1 (positive lower threshold): +162  
(162 codes above mid-scale)
- T2 (negative lower threshold): -162  
(162 codes below mid-scale)
- T3 (positive upper threshold): +32507  
(260 codes below positive full-scale)
- T4 (negative upper threshold): -32508  
(260 codes above negative full-scale)

When in the G = 1 mode, the inner limits, T1 and T2, are used. When an actual ADC result is between T1 and T2, gain is switched to the G = 100 mode. This ensures that the analog input voltage that the ADC sees is maximized as quickly as possible. Then in the G = 100 mode, the outer limits, T3 and T4, are used. If an ADC result is predicted to be above T3 or below T4, the gain is switched to the G = 1 mode to prevent the input of the ADC from being overranged, as shown in Figure 4.

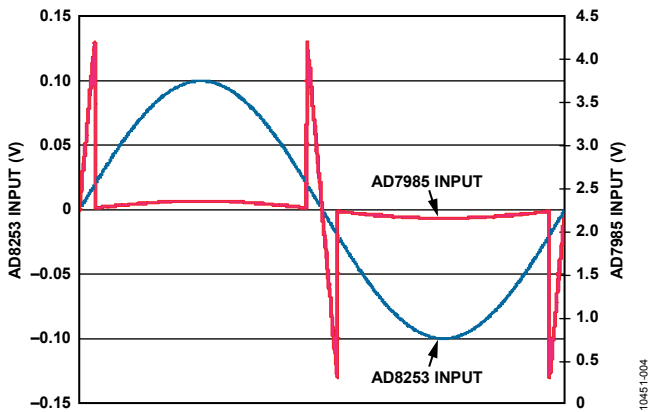


Figure 4. The Gain from the Amplifier Input to the Converter Input Is Reduced by 100 When the Analog-to-Digital Converter Input Is Predicted to Be Outside the Threshold Limits (Blue Line: Amplifier Input; Red Line: Converter Input.)

When in the  $G = 100$  mode, if the algorithm predicts that the next ADC sample would be just outside the outer threshold (using a very rudimentary linear prediction), giving an ADC result of +32510, the gain is switched to  $G = 1$ , so that, instead of +32510, the next ADC result is +325.

**Performance of the Full System**

With fully optimized gain and decimation algorithms, the full system is ready to be tested. Figure 5 shows the system response to a large signal 1 kHz input tone of  $-0.5$  dBFS. When the PGA gain of 100 is factored in, the dynamic range achieved is 127 dB. Similarly, when tested for small signal inputs in Figure 6, with an input tone of 70 Hz @  $-46.5$  dBFS, up to 129 dB of dynamic range is achieved. The improvement in performance at the smaller input tone is expected, as no active switching of gain ranges occurs during this measurement.

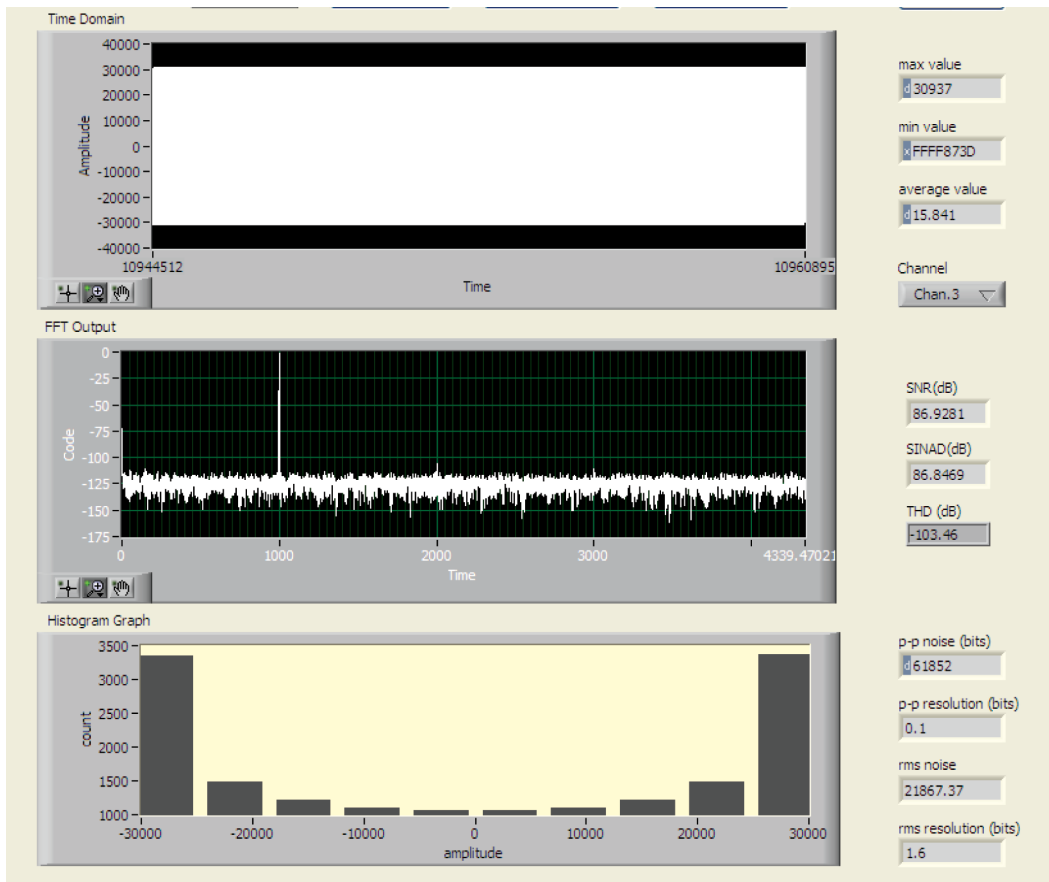


Figure 5. Response to Large-Scale 1 kHz Signal Showing 127 dB Dynamic Range

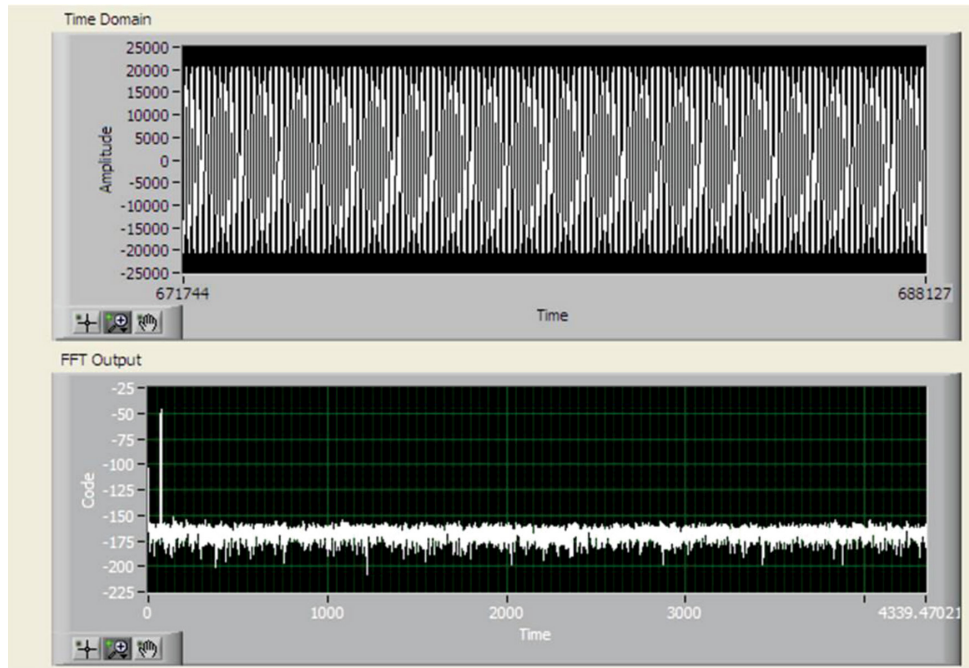


Figure 6. Response to 70 Hz Small-Scale Input Signal

The system's performance relies on the ability to switch the gain dynamically to handle both small- and large-signal inputs. While sigma-delta technology provides excellent dynamic range, the SAR-based solution offers a way to dynamically change the front-end gain based on the input signal, without compromising system performance. This allows both small-signal and large-signal ac and dc inputs to be measured in real time without waiting for system settling time or incurring large glitches due to delayed gain changing.

### COMMON VARIATIONS

Other 16-bit PulSAR ADCs that can be considered for this application are the [AD7983](#) (16-bit @ 1.33 MSPS) and the [AD7980](#) (16-bit @ 1 MSPS). The use of 18-bit PulSAR ADCs is also an option, including the [AD7986](#) (18-bit @ 2 MSPS), [AD7984](#) (18-bit @ 1.33 MSPS), and the [AD7982](#) (18-bit @ 1 MSPS).

### CIRCUIT EVALUATION AND TEST

Figure 3 shows the basic test setup used to evaluate the circuit. A complete schematic and layout of the PCB can be found in the CN-0260 Design Support package found at [www.analog.com/CN0260-DesignSupport](http://www.analog.com/CN0260-DesignSupport).

It is important to use a low noise, low distortion signal source for the input, such as an Agilent 33120A, Audio Precision System Two 2322, or equivalent.

### LEARN MORE

CN0260 Design Support Package:

[www.analog.com/CN0260-DesignSupport](http://www.analog.com/CN0260-DesignSupport)

Ardizzoni, John. "A Practical Guide to High-Speed Printed-Circuit-Board Layout," *Analog Dialogue* 39-09, September 2005.

MT-001 Tutorial, *Taking the Mystery out of the Infamous Formula, "SNR = 6.02N + 1.76dB," and Why You Should Care*, Analog Devices.

MT-004 Tutorial, *The Good, the Bad, and the Ugly Aspects of ADC Input Noise—Is No Noise Good Noise?*, Analog Devices.

MT-021 Tutorial, *ADC Architectures II: Successive Approximation ADCs*, Analog Devices.

MT-022 Tutorial, *ADC Architectures III: Sigma-Delta ADC Basics*, Analog Devices.

MT-031 Tutorial, *Grounding Data Converters and Solving the Mystery of "AGND" and "DGND"*, Analog Devices.

MT-101 Tutorial, *Decoupling Techniques*, Analog Devices.

Colm Slattery and Mick McCarthy, "Oversampled ADC and PGA Combine to Provide 127-dB Dynamic Range," *Analog Dialogue*, Vol.45, December 2011.

**Data Sheets and Evaluation Boards**[System Demonstration Platform \(EVAL-SDP-CB1Z\)](#)[AD7985 Data Sheet](#)[AD8253 Data Sheet](#)[AD8021 Data Sheet](#)[ADA4004-2 Data Sheet](#)[ADR439 Data Sheet](#)**REVISION HISTORY**

1/12—Revision 0: Initial Version

(Continued from first page) Circuits from the Lab circuits are intended only for use with Analog Devices products and are the intellectual property of Analog Devices or its licensors. While you may use the Circuits from the Lab circuits in the design of your product, no other license is granted by implication or otherwise under any patents or other intellectual property by application or use of the Circuits from the Lab circuits. Information furnished by Analog Devices is believed to be accurate and reliable. However, "Circuits from the Lab" are supplied "as is" and without warranties of any kind, express, implied, or statutory including, but not limited to, any implied warranty of merchantability, noninfringement or fitness for a particular purpose and no responsibility is assumed by Analog Devices for their use, nor for any infringements of patents or other rights of third parties that may result from their use. Analog Devices reserves the right to change any Circuits from the Lab circuits at any time without notice but is under no obligation to do so.

©2012 Analog Devices, Inc. All rights reserved. Trademarks and registered trademarks are the property of their respective owners.  
CN10451-0-1/12(0)

[www.analog.com](http://www.analog.com)