



# AN2979

## Application note

---

### Implementing a simple ADC using the STM8L101xx comparator

---

#### Introduction

This application note gives a simple method for implementing an A/D converter with a minimum amount of external components: one resistor and one capacitor.

The practical application example described in this document uses the STM8L101xx microcontroller comparator.

# Contents

- 1      Application description ..... 3**
  - 1.1    Comparator features ..... 3
  - 1.2    ADC implementation ..... 3
  
- 2      Software description ..... 5**
  - 2.1    Application flowcharts ..... 6
  
- 3      Hardware description ..... 7**
  
- 4      Measurements and calibration ..... 8**
  - 4.1    Typical measurements ..... 8
  - 4.2    Precision of the measured value ..... 8
  - 4.3    How to get a better accuracy ..... 9
    - 4.3.1    Hardware solution ..... 9
    - 4.3.2    Software solution ..... 9
  
- 5      Revision history ..... 11**

# 1 Application description

## 1.1 Comparator features

The STM8L101xx microcontroller embeds two zero-crossing comparators sharing the same current bias and the same voltage reference.

This voltage reference can be:

- internal (comparison to ground)
- or external (comparison to a reference pin voltage)

Each comparator is connected to 4 channels which can be used to generate an interrupt, a timer input capture or a timer break. Their polarity can be inverted.

*Note:* For external comparison be aware that the STM8L101xx comparator maximum input value is  $V_{DD} - 1.25\text{ V}$  with  $V_{DDmax} = 3.6\text{ V}$

## 1.2 ADC implementation

Each comparator can be used to implement an ADC. This technique is based on a simple principle: the signal to be measured is connected to the non-inverted input and the reference signal is an external signal connected to the inverting input.

In the demonstration software, the comparator used is COMP2 and the channel used as the signal to be measured is the channel 3 (pin PD2).

The reference signal is generated by charging a capacitor through a resistor. While the voltage across the capacitor is being charged, it follows an exponential curve.

This exponential equation has been implemented in the software. The time taken by the capacitor voltage to rise above the voltage value to be converted is used in the charge equation to retrieve the digital conversion value.

**Charge equation:**

$$V_{\text{meas}} = V_{\text{DD}} \times \left(1 - \exp\left(-\frac{t}{T}\right)\right)$$


Where:

- **Vmeas** is the value to be measured
- **V<sub>DD</sub>** is the input voltage
- **t** is the time measured by timer2 when the comparator detects that the input voltage is above the reference voltage
- **T** is the RC constant (here R=10 kΩ and C=100 nF so T= 1 ms)

The capacitor is charged and discharged using the timer 2 PWM on channel1/ PB0.


A timer is programmed to generate a 2 ms PWM with a duty cycle of 0.25. This 2-ms period permits an ADC implementation using the full voltage range that the comparator tolerates. The capacitor charging curve is shown in the following figure.

**Figure 1. Capacitor charging curve**

 

The figure below shows the connection of the comparator to the required external components.

**Figure 2. Comparator connections**

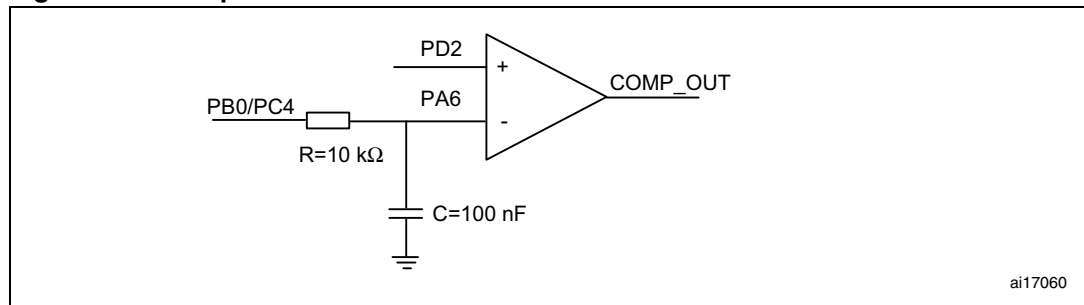

1. Condition:  $V_{DD} = 3.3\text{ V}$ ,  $R = 10\text{ k}\Omega$ ,  $C = 100\text{ nF}$

**Note:** When using the STM8L101-EVAL evaluation board you need to connect the PB0 pin to the PC4 pin. This way you use the resistor and capacitor already present on the board (no hardware needed). Pin PC4 is configured as input floating to avoid any conflict.

## 2 Software description

The software provided with this application note describes a way of implementing an A/D converter (using a timer and analog comparator interrupts).


The application uses four peripherals:

- CLK: the clock enables and provides the correct clock frequency for the peripherals.
- COMP: the comparator detects when the input voltage is above the reference voltage
- TIM2: Timer 2 provides the 2 ms PWM with a duty cycle of 0.25 generating the capacitor charge and discharge. Timer 2 Capture/compare interrupt routine handles the conversion.
- GPIO: the general purpose I/O handles the I/O used.
- SPI: used to communicate with the LCD.

A generic file param.h contains the parameter values that can be modified in order to re-use the application and adapt it easily to other conditions.

At the start, the LCD displays “STM8L ADC using COMP”. Then it continuously displays the measured values.

**Figure 3. Application architecture & description**

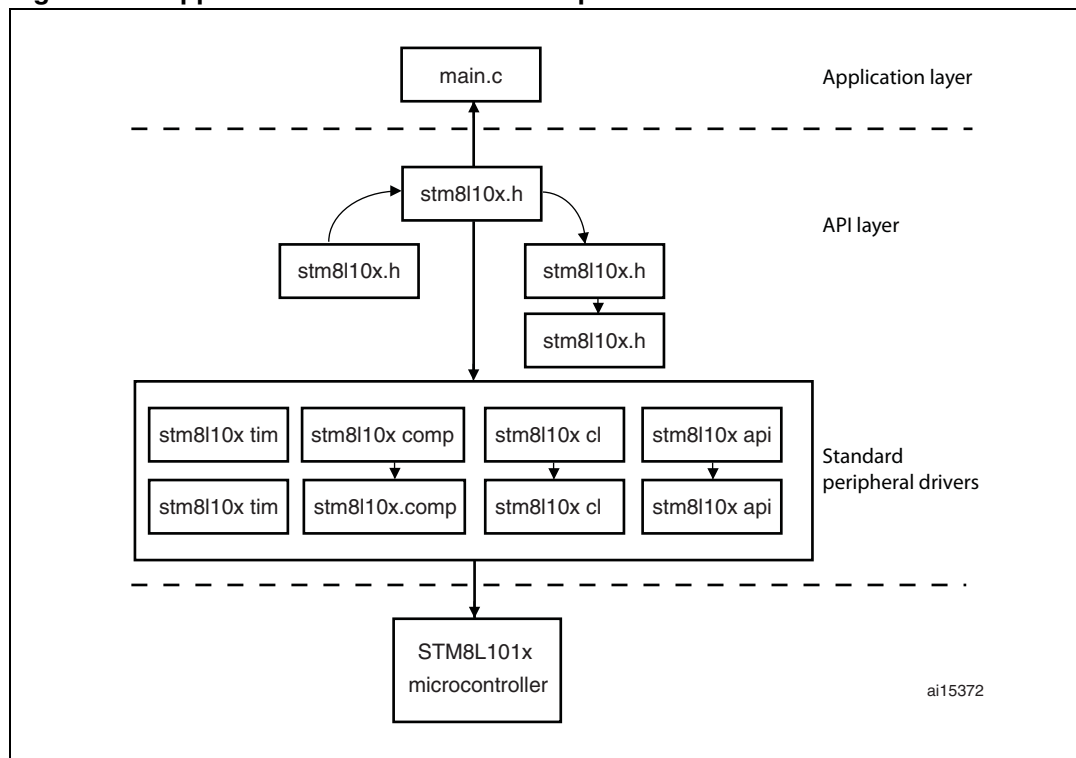

*Note:* The software can be compiled with Cosmic and Raisonance compilers. It contains projects for STVD and Raisonance IDE.

A calibration of some parameters can be optionally set if “#define Calibration” is uncommented in the param.h file.

## 2.1 Application flowcharts

Figure 4. Main loop flowchart



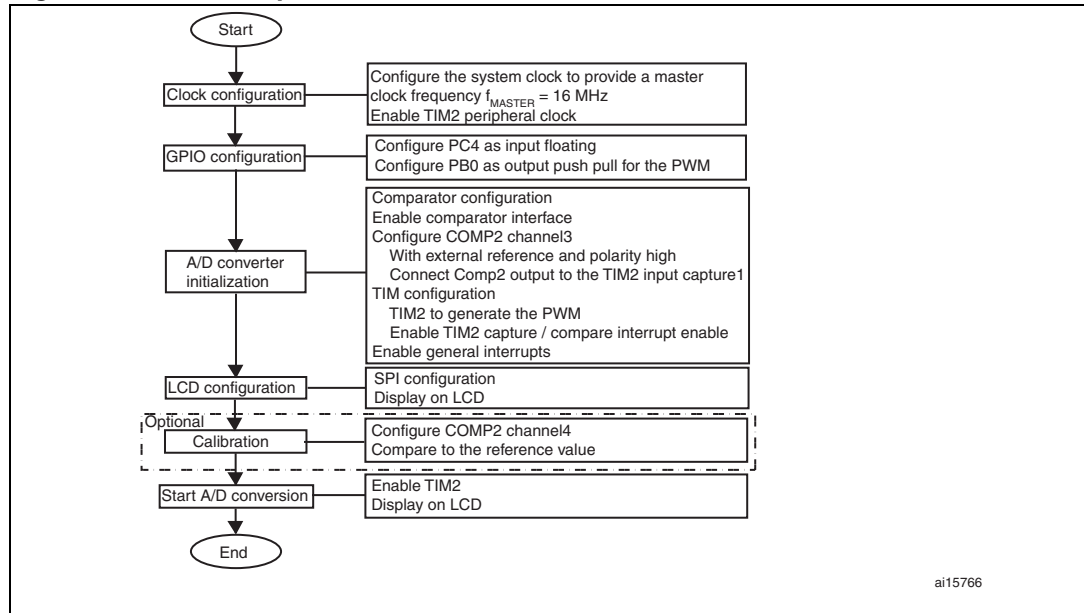


Figure 5. Get conversion value flowchart

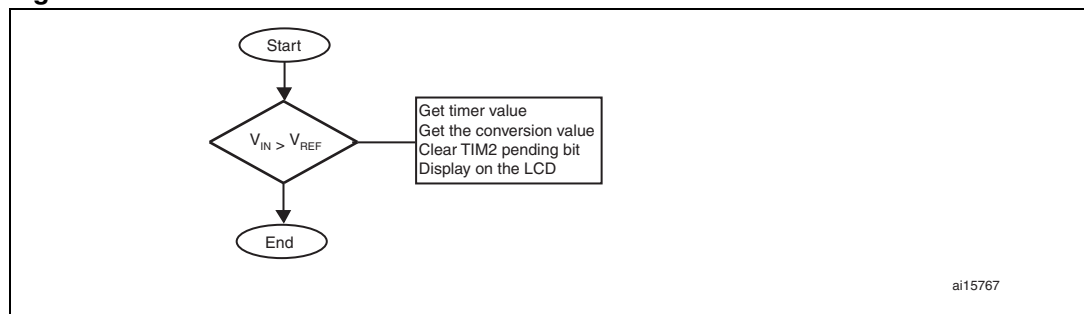

### 3 Hardware description

Figure 6. Circuit diagram

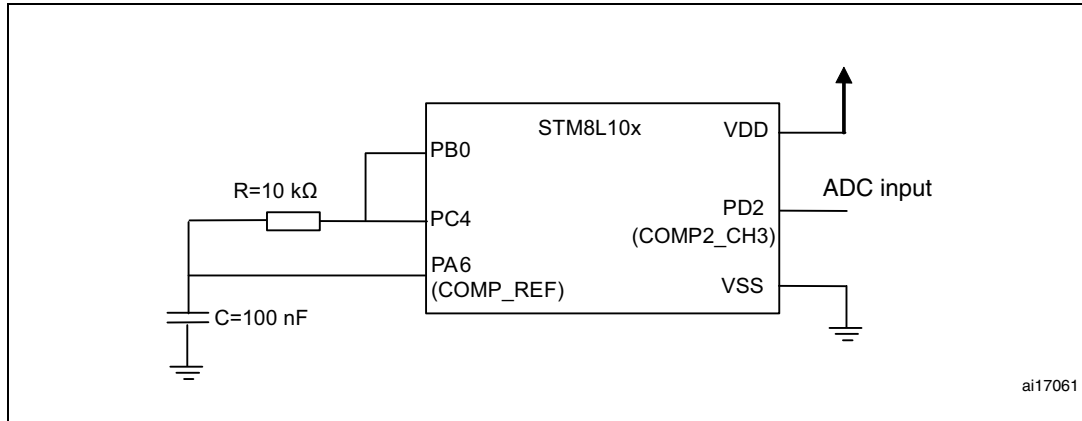

#### STM8L101 evaluation board settings:

- Remove jumper JP2 to connect an external input voltage instead of the potentiometer input. With the potentiometer RV1, the value is limited to 0.8 V and the signal is noisy (due to the LCD). So the display on the LCD screen would not be stable.
- Connect the external ADC voltage input directly to PD2.
- Ground together the evaluation board and the external ADC signal.
- An accurate 3.3 V MCU voltage can be tuned on the evaluation board using RV4.

## 4 Measurements and calibration

### 4.1 Typical measurements

The following values are given for information only.

**Table 1. Measured value after conversion and margin error for  $V_{DD}=3.3$  V**

Value to be measured (V)	Measured value after conversion (V)	Error (%)
0.25	0.204	18.4%
0.5	0.419	16.2%
0.8	0.704	12%
1	0.903	9.7%
1.25	1.14	8.8%
1.5	1.39	7.33%
1.75	1.628	6.97%

### 4.2 Precision of the measured value

When using the RC charge equation, the precision of the measured value depends on the accuracy of the capacitor C and the resistor R.

**Accuracy example:**

if  $C=100$  nF with 10% accuracy:  $C_{acc1}=90$  nF or  $C_{acc2}=110$  nF

if  $R=10$  k $\Omega$  with 2% accuracy:  $R_{acc1}=9.8$  k $\Omega$  or  $R_{acc2}=10.2$  k $\Omega$

**Calculation of the RC constant:**

$$T = R \times C = (10 \times 10^3) \times (100 \times 10^{-9}) = 1 \text{ ms}$$

$$T_{ACC1} = R_{ACC1} \times C_{ACC1} = (9.8 \times 10^3) \times (90 \times 10^{-9}) = 882 \text{ } \mu\text{s}$$

$$T_{ACC2} = R_{ACC2} \times C_{ACC2} = (10.2 \times 10^3) \times (110 \times 10^{-9}) = 1.122 \text{ ms}$$

**Charge equations:**

$$V_{meas} = V_{DD} \times \left(1 - \exp\left(-\frac{t}{T}\right)\right)$$


$$V_{measacc1} = V_{DD} \times \left(1 - \exp\left(-\frac{t}{T_{acc1}}\right)\right)$$

$$V_{measacc2} = V_{DD} \times \left(1 - \exp\left(-\frac{t}{T_{acc2}}\right)\right)$$



The following figure shows the impact of the capacitor and resistor accuracy.

**Figure 7. Charge equation depending on RC accuracy**

 

1. In blue:  $V_{\text{measacc1}}$  ---- In red:  $V_{\text{meas}}$  ---- In green:  $V_{\text{measacc2}}$
2. Condition:  $V_{\text{DD}}=3.3\text{ V}$

**Note:** *The results are not only impacted by the margining error due to hardware components but also by the accuracy of the MCU clock. In this example, the device works at a HSI frequency of 16 MHz at 25 °C, that is, with a clock accuracy of 1% (refer to the datasheet). The temperature variation also impacts the accuracy of the measured value as the microcontroller, resistors and capacitors are temperature dependent.*

## 4.3 How to get a better accuracy

### 4.3.1 Hardware solution

The first solution is to choose components with a high accuracy value (this may imply a higher cost).

### 4.3.2 Software solution

The second solution is to calibrate the RC constant in the software using  $V_{\text{DD}}$  as a reference.


#### Implementation description

In order to perform the calibration, you need to uncomment the "#define calibration" in the "param.h" file.

The calibration is then performed by firmware and the RC constant is updated. This constant is used in the charge equation.

On the STM8L101-EVAL evaluation board, the COMP2 channel 4 (PD3) is connected to  $V_{DD}$  via a resistor bridge.

**Figure 8. Evaluation board calibration schematic**

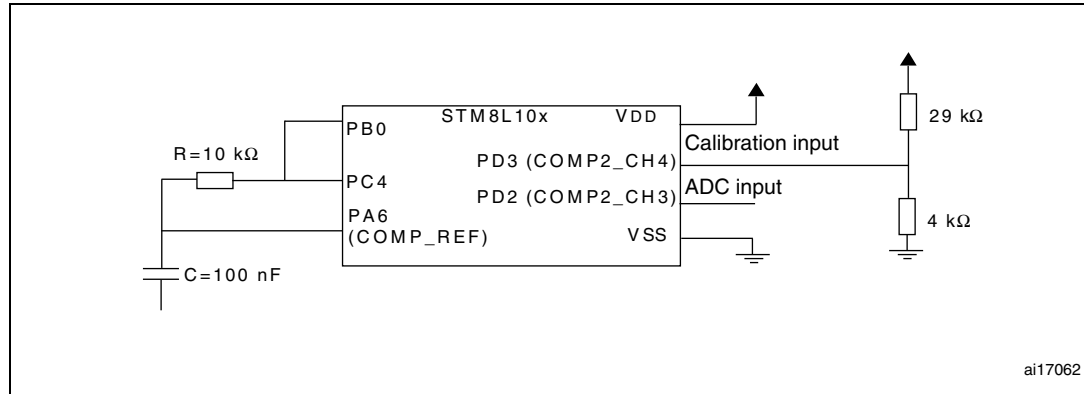

As  $V_{DD}=3.3$  V, PD3 is a fixed value equal to 0.4 V

In the file “param.h” you need to define the “expected\_value” equal to 0.4 ( this value needs to be updated if a different resistor bridge is used).

The specific function “Calibration( )” configures the COMP2 Channel 4 and compares the value measured on this channel with the expected value. This function then updates the RC constant that will be used afterwards.

When the calibration is performed, the COMP2 configuration changes to use the Channel 3 (PD2).

The following table lists a few measurement examples with a calibration performed at  $V_{DD}=3.3$  V,  $R=10$  kΩ and  $C=100$  nF.

**Table 2. Accuracy measurement when the calibration is performed**

Value to be measured (V)	Measured value after conversion (V)	Error (%)
0.25	0.233	6.8%
0.5	0.475	5%
0.8	0.792	1.25%
1	0.99	1%
1.2	1.211	0.92%
1.5	1.512	0.8%
1.75	1.784	1.9%

## 5 Revision history

**Table 3. Document revision history**

Date	Revision	Changes
12-Feb-2010	1	Initial release.

**Please Read Carefully:**

Information in this document is provided solely in connection with ST products. STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, modifications or improvements, to this document, and the products and services described herein at any time, without notice.

All ST products are sold pursuant to ST's terms and conditions of sale.

Purchasers are solely responsible for the choice, selection and use of the ST products and services described herein, and ST assumes no liability whatsoever relating to the choice, selection or use of the ST products and services described herein.

No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted under this document. If any part of this document refers to any third party products or services it shall not be deemed a license grant by ST for the use of such third party products or services, or any intellectual property contained therein or considered as a warranty covering the use in any manner whatsoever of such third party products or services or any intellectual property contained therein.

**UNLESS OTHERWISE SET FORTH IN ST'S TERMS AND CONDITIONS OF SALE ST DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY WITH RESPECT TO THE USE AND/OR SALE OF ST PRODUCTS INCLUDING WITHOUT LIMITATION IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION), OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.**

**UNLESS EXPRESSLY APPROVED IN WRITING BY AN AUTHORIZED ST REPRESENTATIVE, ST PRODUCTS ARE NOT RECOMMENDED, AUTHORIZED OR WARRANTED FOR USE IN MILITARY, AIR CRAFT, SPACE, LIFE SAVING, OR LIFE SUSTAINING APPLICATIONS, NOR IN PRODUCTS OR SYSTEMS WHERE FAILURE OR MALFUNCTION MAY RESULT IN PERSONAL INJURY, DEATH, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE. ST PRODUCTS WHICH ARE NOT SPECIFIED AS "AUTOMOTIVE GRADE" MAY ONLY BE USED IN AUTOMOTIVE APPLICATIONS AT USER'S OWN RISK.**

Resale of ST products with provisions different from the statements and/or technical features set forth in this document shall immediately void any warranty granted by ST for the ST product or service described herein and shall not create or extend in any manner whatsoever, any liability of ST.

ST and the ST logo are trademarks or registered trademarks of ST in various countries.

Information in this document supersedes and replaces all information previously supplied.

The ST logo is a registered trademark of STMicroelectronics. All other names are the property of their respective owners.

© 2010 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia - Malta - Morocco - Philippines - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

[www.st.com](http://www.st.com)